

# REGISTER TRANSFER AND MICROOPERATIONS

- Register Transfer Language
- Register Transfer
- Bus and Memory Transfers
- Arithmetic Microoperations
- Logic Microoperations
- Shift Microoperations
- Arithmetic Logic Shift Unit

*Compute*

Register

$\mu\text{-op}$

2


Register

$r$

# MICROOPERATION

An elementary operation performed during one clock pulse, on the information stored in one or more registers

Compute

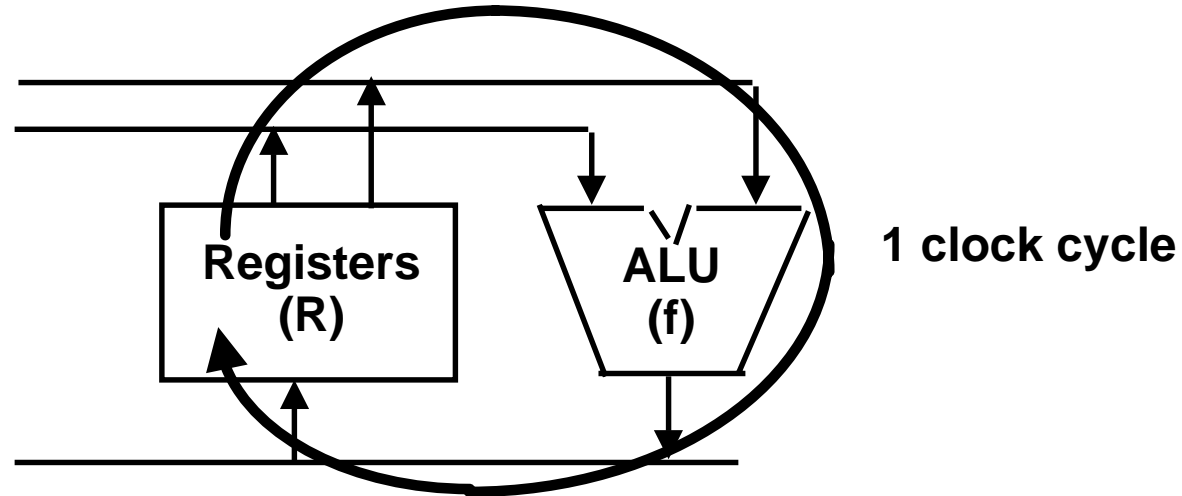

$$R \leftarrow f(R, R)$$

f: shift, count, clear, load, add,...

o  
r

# REGISTER TRANSFER LANGUAGE

## Definition of the organization of a computer

- Set of registers and their functions
- ~~Microoperations Set~~  
Set of allowable microoperations provided by the organization of the computer
- Control signals that initiate the sequence of microoperations

For any function of the computer, a sequence of microoperations is used to describe it

----> *Regi*

- A symbolic language
- A convenient tool for describing the internal organization of digital computers
- Can also be used to facilitate the design process of digital systems.


r

# REGISTER TRANSFER

- Designation of a register**
- a register
  - portion of a register
  - a bit of a register


**Common ways of drawing the block diagram of a register**

Register

 

Numbering of bits

Showing individual bits

 

Subfields

**Representation of a transfer(parallel)**

$$R2 \leftarrow R1$$

*Compute*

A simultaneous transfer of all bits from the source to the destination register, during one clock pulse

**Representation of a controlled(conditional) transfer**

$$P: R2 \leftarrow R1$$

A binary condition( $p=1$ ) which determines when the transfer is to occur


$$\text{If } (p=1) \text{ then } (R2 \leftarrow R1)$$

# HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS


## Implementation of controlled transfer

P:  $R2 \leftarrow R1$

### Block diagram

 

### Timing diagram

 

### Compute

## Basic Symbols for Register Transfers


Symbols and numerals	Description	Meaning
Parentheses ( )	Denotes a part of a register	$R2(0-7)$ , $R2(L)$
Arrow $\leftarrow$	Denotes transfer of information	$R2 \leftarrow R1$
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	$A \leftarrow B$ , $B \leftarrow A$
Capital letters	Denotes a register	MAR, R2

r

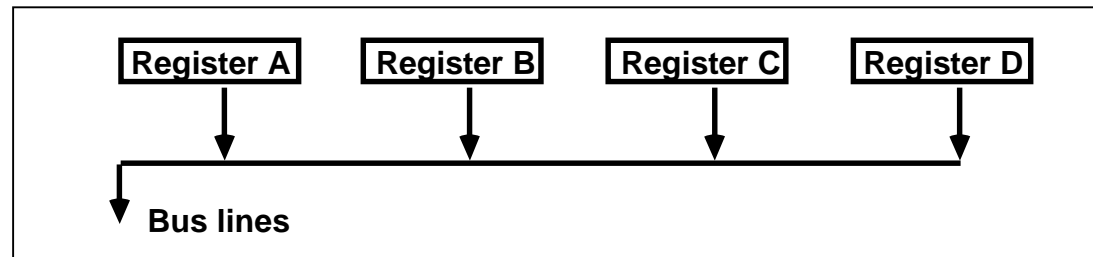
# BUS AND MEMORY TRANSFER

Bus is a path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations.


From a register to bus:  $BUS \leftarrow R$



Compute

 

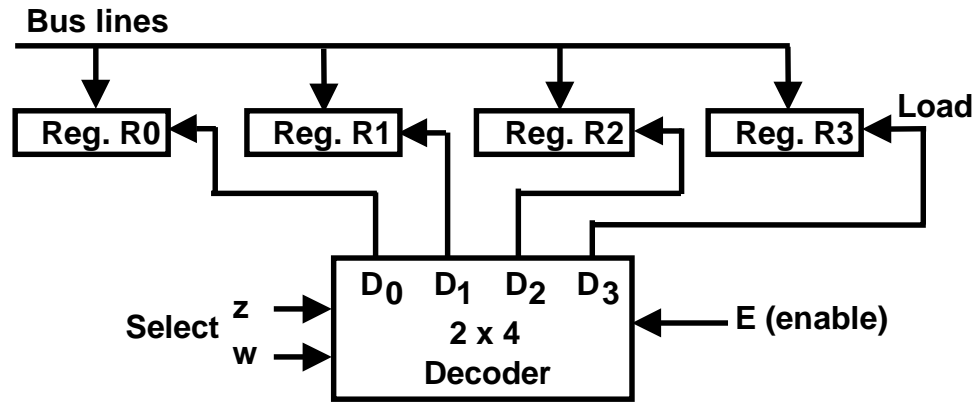
# TRANSFER FROM BUS TO A DESTINATION REGISTER



## Three-State Bus Buffers


Normal input A  
Control input C

 

Output  $Y=A$  if  $C=1$   
High-impedence if  $C=0$


Compute

## Bus line with three-state buffers

 

$r$ 

# MEMORY TRANSFERS

 

Memory *read* micro-op:  $DR \leftarrow M$       ( $DR \leftarrow M[AR]$ )  
 Memory *write* micro-op:  $M \leftarrow DR$       ( $M[AR] \leftarrow DR$ )

## Summary of Register Transfer Microoperations

Compute

$A \leftarrow B$   
 $AR \leftarrow DR(AD)$   
 $A \leftarrow \text{constant}$   
 $ABUS \leftarrow R1,$   
 $R2 \leftarrow ABUS$   
 AR  
 DR  
 $M[R]$   
 M  
 $DR \leftarrow M$   
  
 $M \leftarrow DR$

Transfer content of reg. B into reg. A  
 Transfer content of AD portion of reg. DR into reg. AR  
 Transfer a binary constant into reg. A  
 Transfer content of R1 into bus A and, at the same time,  
 transfer content of bus A into R2  
 Address register  
 Data register  
 Memory word specified by reg. R  
 Equivalent to  $M[AR]$   
 Memory *read* operation: transfers content of  
 memory word specified by AR into DR  
 Memory *write* operation: transfers content of  
 DR into memory word specified by AR



r

# ARITHMETIC MICROOPERATIONS

## Four types of microoperations

- Register transfer microoperations
- Arithmetic microoperations
- Logic microoperations
- Shift microoperations

## \* Summary of Arithmetic Micro-Operations

Compute

$$R3 \leftarrow R1 + R2$$

Contents of R1 plus R2 transferred to R3

$$R3 \leftarrow R1 - R2$$

Contents of R1 minus R2 transferred to R3

$$R2 \leftarrow R2'$$

Complement the contents of R2

$$R2 \leftarrow R2' + 1$$

2's complement the contents of R2 (negate)

$$R3 \leftarrow R1 + R2' + 1$$

subtraction

$$R1 \leftarrow R1 + 1$$

Increment

$$R1 \leftarrow R1 - 1$$

Decrement

Register

$\mu$ -op


10

Ar


r

# BINARY ADDER


## Binary Adder

 

## Binary Adder-Subtractor

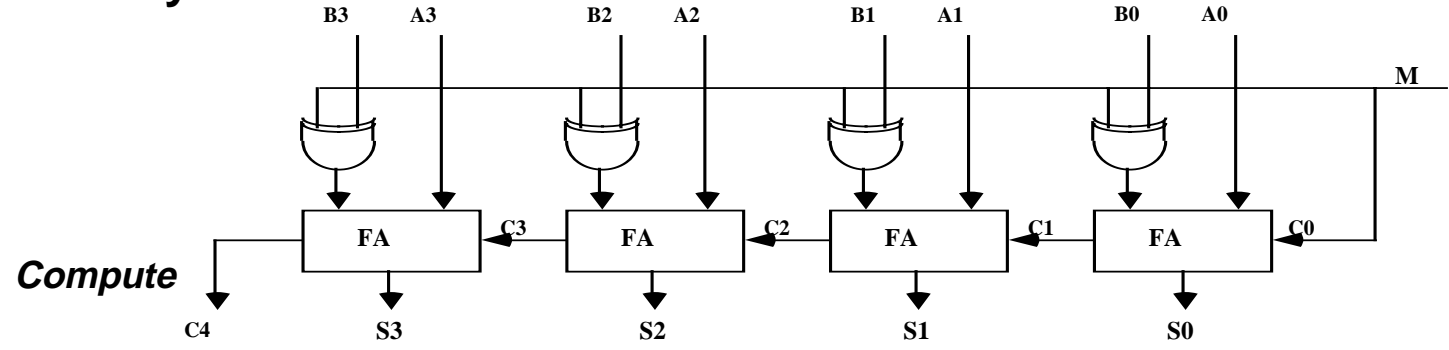

## Binary Incrementer

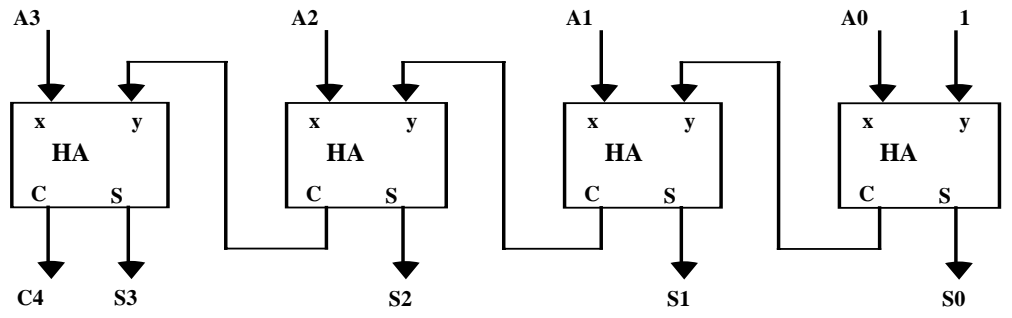

Register


$\mu$ -op

11

Ar

r

# ARITHMETIC CIRCUIT

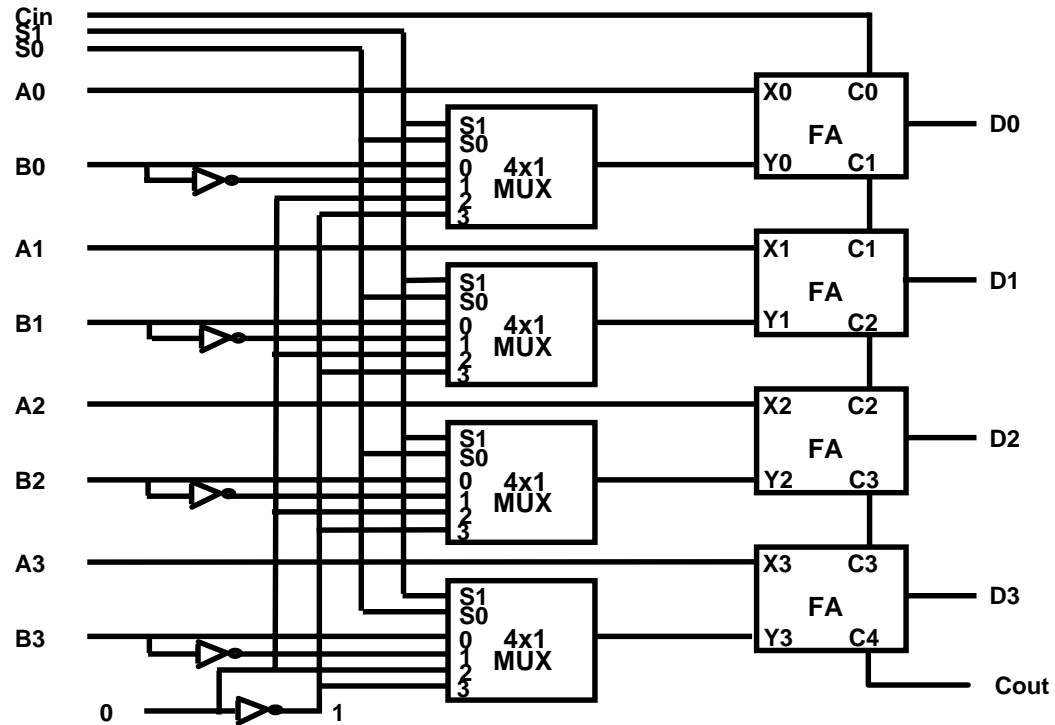

Compute

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

o  
r

# LOGIC MICROOPERATIONS

Specify binary operations on the strings of bits in registers.

- useful for bit manipulations on binary data

AND: Mask out certain group of bits

OR : Merge binary or character data

- useful for making logical decisions based on the bit value

## Applications

Manipulating individual bits or a field(portion) of a word in a register

*Compute*


- |                        |                   |
|------------------------|-------------------|
| - Selective-set        | $A + B$           |
| - Selective-complement | $A \oplus B$      |
| - Selective-clear      | $A \cdot \bar{B}$ |
| - Mask (Delete)        | $A \cdot B$       |
| - Insert               | $(A \cdot B) + C$ |
| - Compare              | $A \oplus B$      |
| - Packing              | $(A \cdot B) + C$ |
| - Unpacking            | $A \cdot B$       |

# LIST OF LOGIC MICROOPERATIONS

- List of Logic Micro-Operations
  - 16 different logic operations with 2 binary vars.
  - n binary vars  $\rightarrow 2^{2^n}$  functions
- Truth tables for 16 functions of 2 variables and the corresponding 16 logic micro-operations

x	y	Boolean Function	Micr	
0	0	F0 = 0	F ← 0	Clear
0	0	F1 = xy	F ← A ∧ B	AND
0	0	F2 = xy'	F ← A ∧ B'	
0	0	F3 = x	F ← A	Transfer A
0	1	F4 = x'y	F ← A' ∧ B	
0	1	F5 = y	F ← B	Transfer B
0	1	F6 = x ⊕ y	F ← A ⊕ B	Exclusive-OR
0	1	F7 = x + y	F ← A ∨ B	OR
1	0	F8 = (x + y)'	F ← (A ∨ B)'	NOR
1	0	F9 = (x ⊕ y)'	F ← (A ⊕ B)'	Exclusive-NOR
1	0	F10 = y'	F ← B'	Complement B
1	0	F11 = x + y'	F ← A ∨ B	
1	1	F12 = x'	F ← A'	Complement A
1	1	F13 = x' + y	F ← A' ∨ B	
1	1	F14 = (xy)'	F ← (A ∧ B)'	NAND
1	1	F15 = 1	F ← all 1's	Set to all 1's
 
# HARDWARE IMPLEMENTATION OF LOGIC MICROOPERATIONS



Compute

Function table

$S_1$	$S_0$	Output	$\mu$ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement

0  
r rc


# SHIFT MICROOPERATIONS

## Shifts

- *Log* : shift in a 0 into the extreme flip-flop
- *Ci* : circulates the bits of the register around the two ends
- *Arith* : shifts a signed number (shift with sign extension)  
 Left shift -> multiplied by 2  
 Right shift -> divided by 2

## Arithmetic shifts for signed binary numbers

### - Arithmetic shift-right

 


Compute - Arithmetic shift-left Overflow  $V = R_{n-1} \neq R_{n-2}$

## Shift Micro-Operations

<i>Sy</i>	
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular right-shift register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left register R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right register R

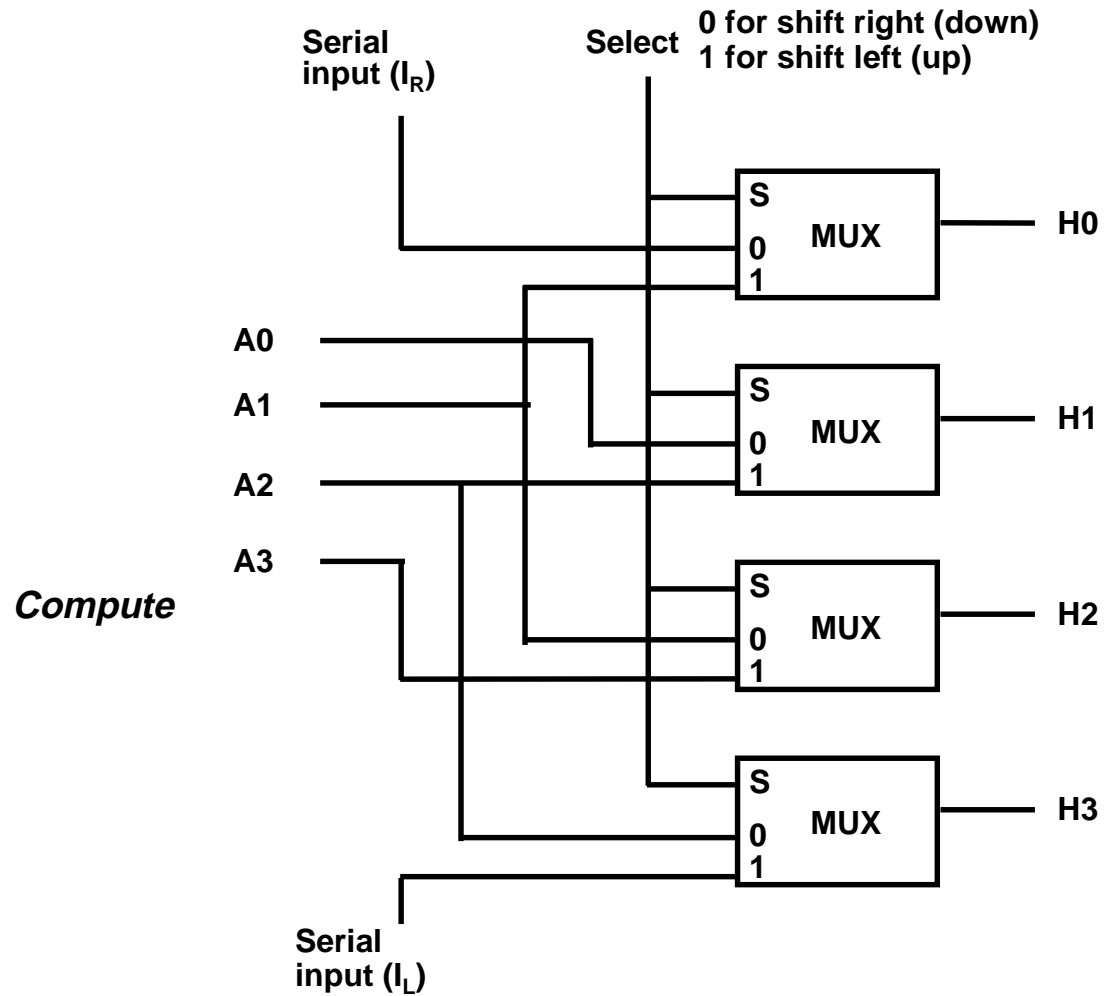
# HARDWARE IMPLEMENTATION OF SHIFT MICROOPERATIONS





r

# ARITHMETIC LOGIC SHIFT UNIT

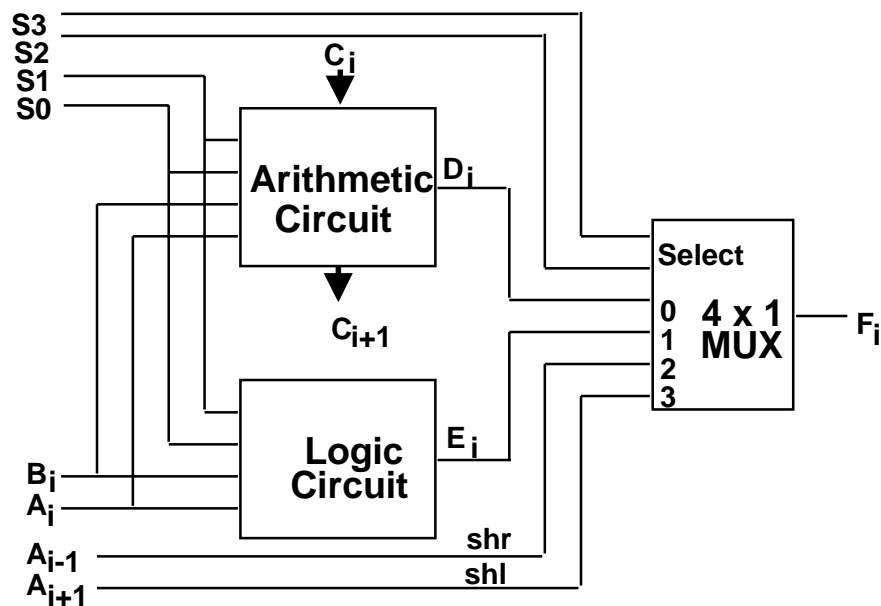

	S3	S2	S1	S0	Cin	Operation	Function
Compute	0	0	0	0	0	$F = A$	Transfer A
	0	0	0	0	1	$F = A + 1$	Increment A
	0	0	0	1	0	$F = A + B$	Addition
	0	0	0	1	1	$F = A + B + 1$	Add with carry
	0	0	1	0	0	$F = A + B'$	Subtract with borrow
	0	0	1	0	1	$F = A + B' + 1$	Subtraction
	0	0	1	1	0	$F = A - 1$	Decrement A
	0	0	1	1	1	$F = A$	Transfer A
	0	1	0	0	X	$F = A \wedge B$	AND
	0	1	0	1	X	$F = A \vee B$	OR
	0	1	1	0	X	$F = A \oplus B$	XOR
	0	1	1	1	X	$F = A'$	Complement A
	1	0	X	X	X	$F = \text{shr } A$	Shift right A into F
	1	1	X	X	X	$F = \text{shl } A$	Shift left A into F