

# **2 Boolean Algebra and Logic Gates**

---

**2.1**

**2.2**

**2.3**

**2.4**

**2.5**

**2.6**

**2.7**

**2.8 IC**

# Boolean Algebra

□ 1854 George Boole

□ 가

가 2	$x+0 = x$	$x \cdot 1 = x$
가 5	$x+x' = 1$	$x \cdot x' = 0$
1	$x+x = x$	$x \cdot x = x$
2	$x+1 = 1$	$x \cdot 0 = 0$
3,	$(x')' = x$	$(x')' = x$
가 3,	$x+y = y+x$	$xy = yx$
4,	$x+(y+z) = (x+y)+z$	$x(yz) = (xy)z$
가 4,	$x(y+z) = xy+xz$	$x+yz = (x+y)(x+z)$
5, De Morgan	$(x+y)' = x'y'$	$(xy)' = x'+y'$
6,	$x+xy = x$	$x(x+y) = x$

# Duality Principle

---

□ AND  $\Leftrightarrow$  OR, 0  $\Leftrightarrow$  1

□

“ 가 ” ( )

(ex)  $x+xy = x$

$$x(x+y) = x$$

□

“ ”

(ex)  $f = x(y'z + yz)$   $f$

dual of  $f = x+(y' + z')(y+z)$

therefore,  $f = x' + (y+z)(y' + z')$

1. 가

$$(ex) x+yz = (x+y)(x+z)$$

$$= xx+xz+xy+yz = x1+xz+xy+yz = x(1+z+y)+yz = x+yz$$

=



2.

x	y	z	yz	x+yz	x+y	x+z	(x+y)(x+z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

( )

### 3. Venn Diagram

(ex)  $x+yz = (x+y)(x+z)$

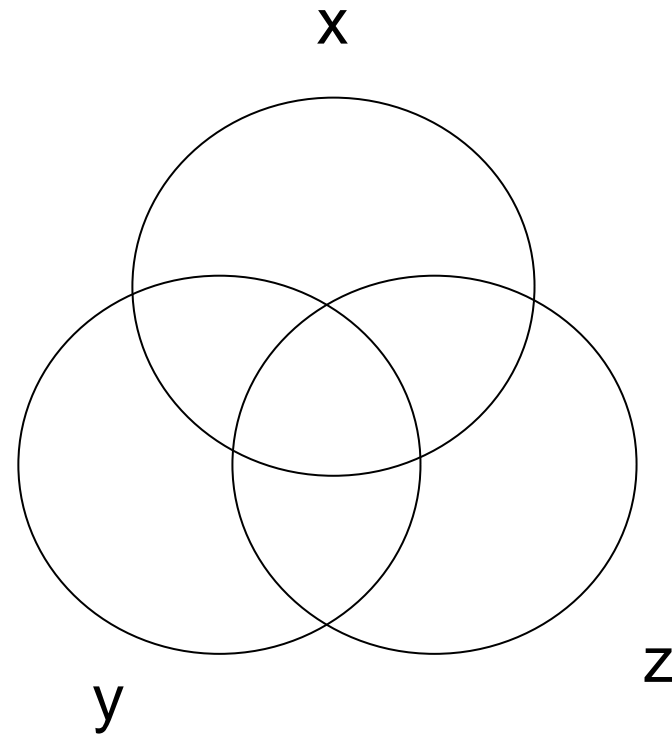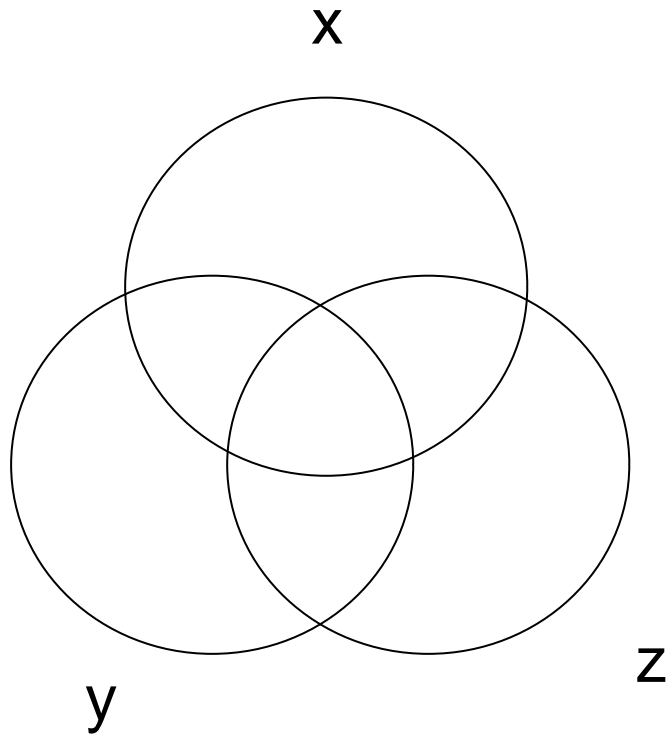



# Boolean Function

- : NOT AND OR
- 

x	y	z	F <sub>1</sub>	F <sub>2</sub>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1

$$F_1 = xyz'$$
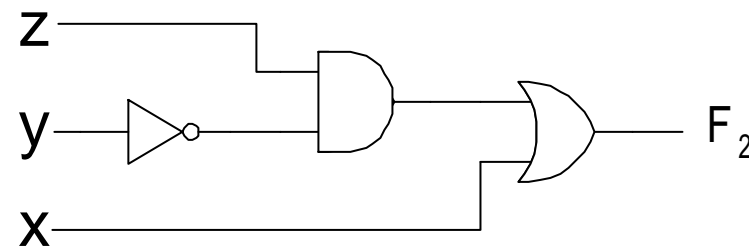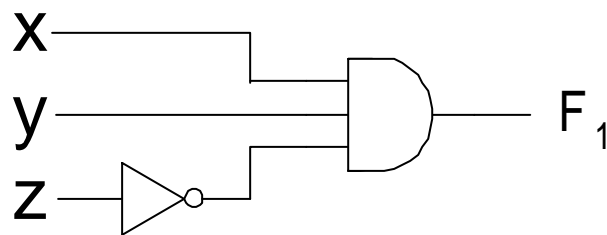
$$\begin{aligned}
 F_2 &= x'y'z + xy'z' + xy'z + xyz' + xyz \\
 &= x'y'z + xy'(z' + z) + xy(z' + z) = x'y'z + xy' + xy \\
 &= x'y'z + x(y' + y) = x'y'z + x = (x' + x)(y'z + x) \\
 &= x + y'z
 \end{aligned}$$





# Boolean Function

x	y	z	F <sub>3</sub>	F <sub>4</sub>
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0



$$\begin{aligned}
 F_3 &= x' y' z + x' y z + x y' z' + x y' z \\
 &= x' y' z + x' y z + x y' (z' + z) \\
 &= x' y' z + x' y z + x y'
 \end{aligned}$$
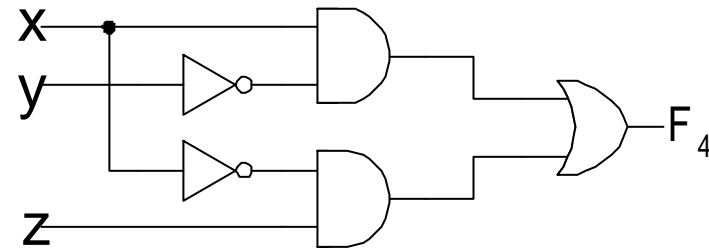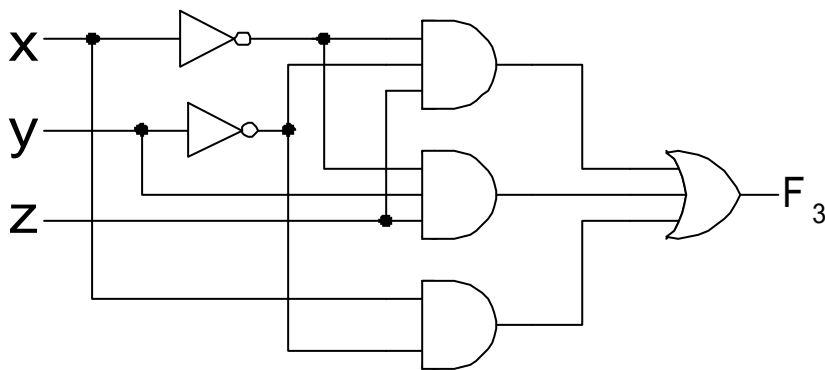
$$\begin{aligned}
 F_4 &= x' y' z + x' y z + x y' z' + x y' z = x' y' z + x' y z + x y' (z' + z) \\
 &= x' y' z + x' y z + x y' = x' z (y' + y) + x y' \\
 &= x' z + x y'
 \end{aligned}$$



# Gate Diagram

$$F = x' y' z + x' y z + x y'$$

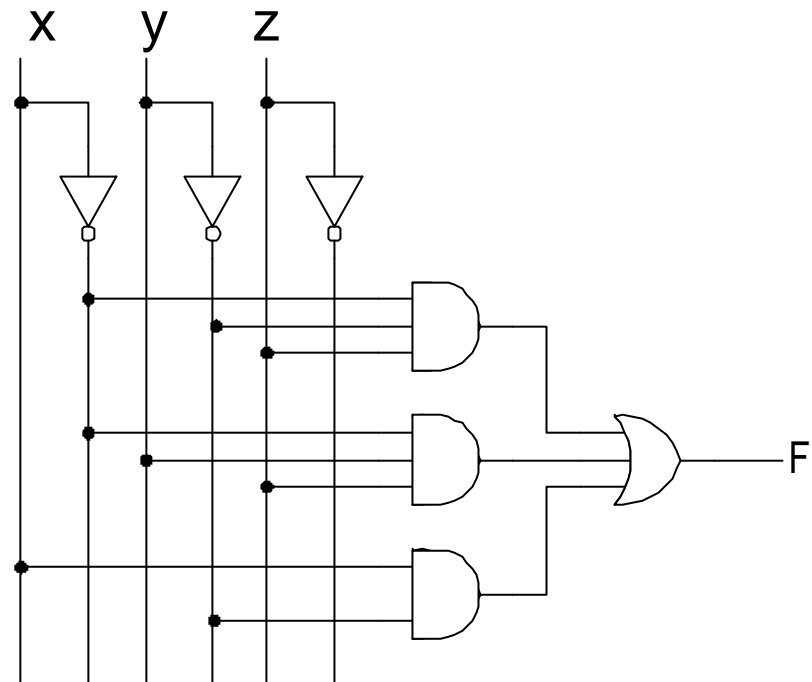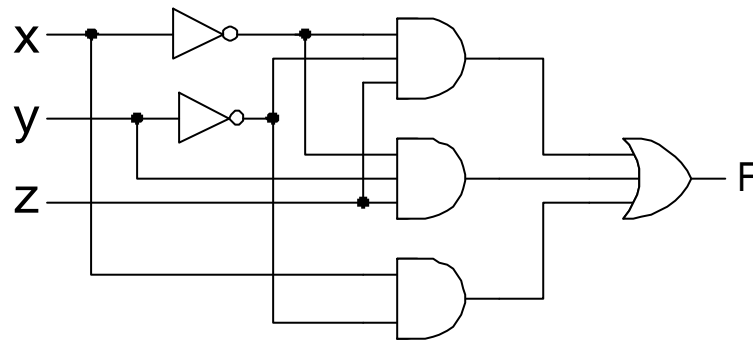



# Minimization of Boolean Function


□

□


literal

,

Literal : prime

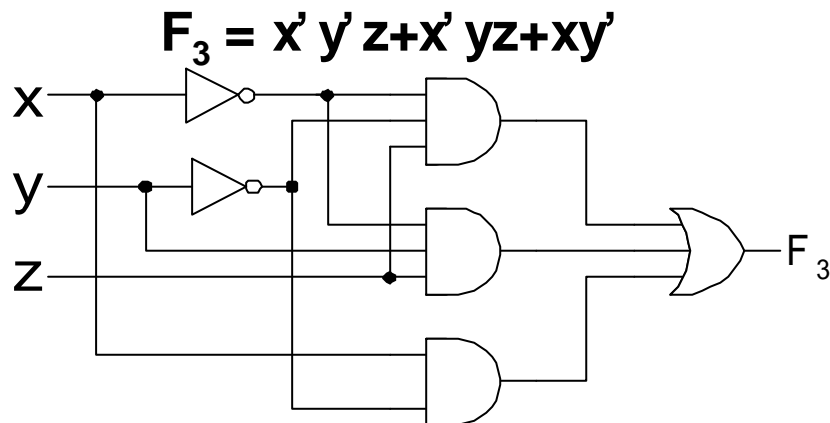

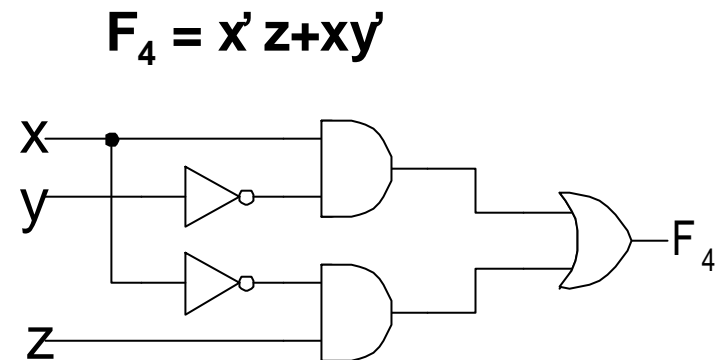- : 6
- 2- AND : 1, 3- AND : 2
- 3- OR : 1, NOT : 2
- Literal : 8



- : 5
- 2- AND : 2, 2- OR : 1,
- NOT : 2
- Literal : 4

# Complement of Boolean Function

---

## 1. De Morgan

$$\text{(ex) } f_1 = x' yz' + x' y' z$$

$$\begin{aligned} f_1' &= (x' yz' + x' y' z)' \\ &= (x' yz')' (x' y' z)' \\ &= (x+y'+z)(x+y+z') \end{aligned}$$

$$f_2 = x(y' z' + yz)$$

$$\begin{aligned} f_2' &= [x(y' z' + yz)]' \\ &= x' + (y' z' + yz)' \\ &= x' + (y' z')' (yz)' \\ &= x' + (y+z)(y' + z') \end{aligned}$$

## 2. Duality

$$\text{(ex) } f_1 = x' yz' + x' y' z$$

$$\text{dual of } f_1 = (x' + y + z')(x' + y' + z)$$

$$\text{therefore, } f_1' = (x + y' + z)(x + y + z')$$

$$f_2 = x(y' z' + yz)$$

$$\text{dual of } f_2 = x + (y' + z')(y + z)$$

$$\text{therefore, } f_2' = x' + (y + z)(y' + z')$$

# Canonical Form : sum of minterms, product of maxterms

□ n bit  $2^n$

- ◆ minterm : AND 가 “1”
- ◆ Maxterm : OR 가 “0”

□ 가 3

x y z	Minterm		Maxterm	
0 0 0	$x'y'z'$	$m_0$	$x+y+z$	$M_0$
0 0 1	$x'y'z$	$m_1$	$x+y+z'$	$M_1$
0 1 0	$x'yz'$	$m_2$	$x+y'+z$	$M_2$
0 1 1	$x'yz$	$m_3$	$x+y'+z'$	$M_3$
1 0 0	$xy'z'$	$m_4$	$x'+y+z$	$M_4$
1 0 1	$xy'z$	$m_5$	$x'+y+z'$	$M_5$
1 1 0	$xyz'$	$m_6$	$x'+y'+z$	$M_6$
1 1 1	$xyz$	$m_7$	$x'+y'+z'$	$M_7$

$$m_i' = M_i$$

$$M_i' = m_i$$

# Minterm & Maxterm

	$m_0$			$m_4$			$M_0$		$M_4$	
x	y	z	$x'y'z'$	$xy'z'$	$m_0+m_4$	$x+y+z$	$x'+y+z$	$M_0M_4$		
0	0	0	1	0	1	0	1	0		
0	0	1	0	0	0	1	1	1		
0	1	0	0	0	0	1	1	1		
0	1	1	0	0	0	1	1	1		
1	0	0	0	1	1	1	0	0		
1	0	1	0	0	0	1	1	1		
1	1	0	0	0	0	1	1	1		
1	1	1	0	0	0	1	1	1		

$$m_k = \overline{M_k}$$

$$m_0+m_4 = \overline{M_0M_4}$$

$$m_0+m_4 = \dot{a} (0,4) = \tilde{O} (1,2,3,5,6,7)$$

0,4      "1" = 1,2,3,5,6,7      "0"

$$M_0M_4 = \tilde{O} (0,4) = \dot{a} (1,2,3,5,6,7)$$

1,2,3,5,6,7      "1" = 0,4      "0"

# Minterm and Maxterm

x	y	z	$f_1$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$f_1 = x' y' z + x y' z' + x y z = m_1 + m_4 + m_7 = \mathbf{\dot{a}(1,4,7)}$$

$$f_1' = (m_1 + m_4 + m_7)' = m_1' m_4' m_7' = M_1 M_4 M_7 = \mathbf{\tilde{O}(1,4,7)}$$

$$f_1' = x' y' z' + x' y z' + x' y z + x y' z + x y z' = m_0 + m_2 + m_3 + m_5 + m_6 = \mathbf{\dot{a}(0,2,3,5,6)}$$

$$f_1 = (f_1')' = (m_0 + m_2 + m_3 + m_5 + m_6)' = m_0' m_2' m_3' m_5' m_6' = M_0 M_2 M_3 M_5 M_6 = \mathbf{\tilde{O}(0,2,3,5,6)}$$

Therefore,

$$f_1 = \mathbf{\dot{a}(1,4,7) = \tilde{O}(0,2,3,5,6)}$$

$$= x' y' z + x y' z' + x y z = (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z')(x'+y'+z)$$

$$f_1' = \mathbf{\dot{a}(0,2,3,5,6) = \tilde{O}(1,4,7)}$$

$$= x' y' z' + x' y z' + x' y z + x y' z + x y z' = (x+y+z')(x'+y+z)(x'+y'+z')$$

# Minterm & Maxterm

x	y	z	g
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$g = \sum (0,4) = x' y' z + x y' z$$

0,4                      "1"

1,2,3,5,6,7                      "0"

$$g = \sum (0,4)$$

$$= \prod (1,2,3,5,6,7)$$

x	y	z	g'
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$g' = \prod (0,4) = (x+y+z)(x'+y+z) = y+xz+x'y+y+yz+x'z+yx+z$$

$$= y(x+x'+1+z+x)+z(x+x'+1)+xy = y+z+xy = y(1+x)+z$$

$$= y+z$$

0,4                      "0"

1,2,3,5,6,7                      "1"

$$g' = \prod (0,4)$$

$$= \sum (1,2,3,5,6,7)$$

# Minterm and Maxterm

---

x	y	z	$f_2$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$f_2 = \mathbf{\dot{a}} ( \quad ) : \text{sum of minterm}$$
$$= \mathbf{\tilde{O}} ( \quad ) : \text{product of maxterm}$$

$$f_2' = \mathbf{\dot{a}} ( \quad ) : \text{sum of minterm}$$
$$= \mathbf{\tilde{O}} ( \quad ) : \text{product of maxterm}$$

# Sum of Minterm

---

$$f_1(A,B,C) = A+B' C$$

1.

$$\begin{aligned} f_1 &= A+B' C \\ &= A(B+B') + B' C(A'+A) \\ &= AB+AB' +A' B' C+AB' C \\ &= AB(C+C') + AB' (C+C') + A' B' C+AB' C \\ &= ABC+ABC' +AB' C+AB' C' +A' B' C+AB' C \\ &= ABC+ABC' +AB' C+AB' C' +A' B' C \\ &= m_7+m_6+m_5+m_4+m_1 \\ &= \mathbf{\dot{a} (1,4,5,6,7)} \end{aligned}$$

2.

A	B	C	f <sub>1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned} f_1 &= m_1 + m_4+m_5+m_6+ m_7 \\ &= \mathbf{\dot{a} (1,4,5,6,7)} \end{aligned}$$



# Product of Maxterm

$$f_1(A,B,C) = A+B' C$$

1.

$$\begin{aligned} f_1 &= A+B' C \\ &= (A+B')(A+C) \\ &= (A+B'+CC')(A+C+BB') \\ &= (A+B'+C)(A+B'+C')(A+C+B)(A+C+B') \\ &= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C) \\ &= (A+B'+C)(A+B'+C')(A+B+C) \\ &= M_2 M_3 M_0 \\ &= \tilde{O}(0,2,3) \end{aligned}$$

2.

A	B	C	f <sub>1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned} f_1 &= m_1 + m_4 + m_5 + m_6 + m_7 \\ &= \mathbf{a}(1,4,5,6,7) \\ &= \tilde{O}(0,2,3) \end{aligned}$$

# Sum of Minterm, Product of Maxterm

$$f(x,y,z) = xy + x'z$$


x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$f = \sum (1,3,6,7)$$


$$= \prod (0,2,4,5)$$

$$f = \sum (1,3,6,7) = x'y'z + x'yz + xyz' + xyz$$
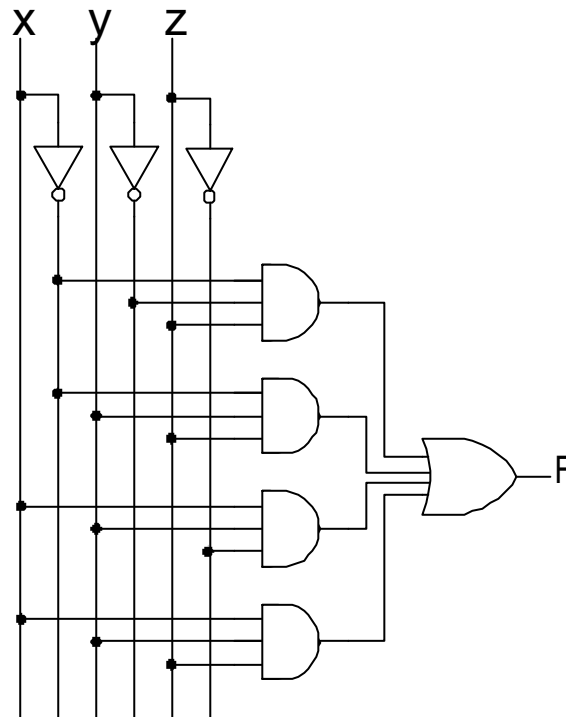
$$f = \prod (0,2,4,5) = (x+y+z)(x+y'+z)(x'+y+z)(x'+y+z')$$



$$f = \sum (1,3,6,7)$$

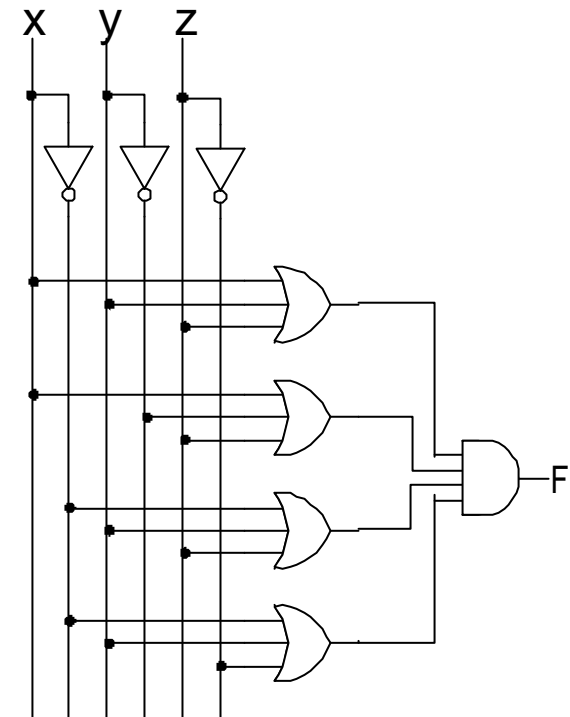

$$f = \prod (0,2,4,5)$$

# Standard Form : sum of products, product of sums

---

□ Sum of products : (AND) (OR)

$$(ex) f = y' + xy + x' yz$$

□ Product of sums : (OR) (AND)

$$(ex) f = x(y' + z)(x + y' + z)$$

canonical form(sum of minterm, product of maxterm)

standard form

□ : 가





가

$$(ex) f = (ab+cd)(a' b' +c' d')$$





$$= aba' b' +abc' d' +a' b' cd+cdc' d'$$

$$= abc' d' +a' b' cd$$

# Digital Logic Gates

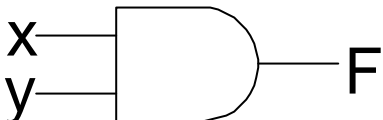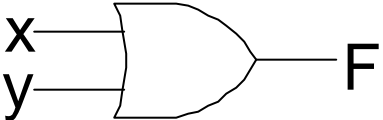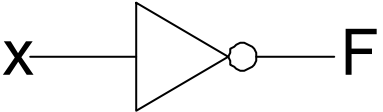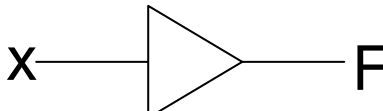Name	Graphic symbol	Algebraic function	Truth Table															
<b>AND</b>		$F = xy$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	X	Y	F	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
<b>OR</b>		$F = x+y$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
<b>NOT (inverter)</b>		$F = x'$	<table border="1"> <thead> <tr> <th>X</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	X	F	0	1	1	0									
X	F																	
0	1																	
1	0																	
<b>Buffer</b>		$F = x$	<table border="1"> <thead> <tr> <th>X</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> </tr> </tbody> </table>	X	F	0	0	1	1									
X	F																	
0	0																	
1	1																	

# Digital Logic Gates

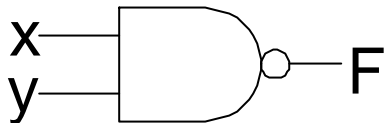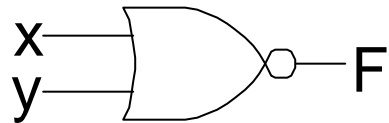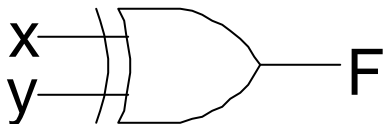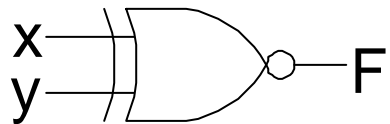Name	Graphic symbol	Algebraic function	Truth Table															
<b>NAND</b>		$F = (xy)'$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
<b>NOR</b>		$F = (x+y)'$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
<b>XOR</b>		$F = x'y + xy'$ $= x \oplus y$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
<b>XNOR</b>		$F = xy + x'y'$ $= x \odot y$	<table border="1"> <thead> <tr> <th>X</th> <th>Y</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

/

□ AND, OR, XOR, XNOR : /

□ NAND, NOR :


AND	$xy = yx$	$(xy)x = x(yz)$
OR	$x+y = y+x$	$(x+y)+z = x+(y+z)$
XOR	$x \oplus y = y \oplus x$	$(x \oplus y) \oplus z = x \oplus (y \oplus z)$
XNOR	$x \odot y = y \odot x$	$(x \odot y) \odot z = x \odot (y \odot z)$
NAND	$(xy)' = (yx)'$	$[(xy)'z]' \quad [x(yz)']'$
NOR	$(x+y)' = (y+x)'$	$[(x+y)'+z]' \quad [x+(y+z)']'$

# XOR Gate


□ XOR

(odd function) : “1” 가 “1”

A	B	C	$A \oplus B$	$A \oplus B \oplus C$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

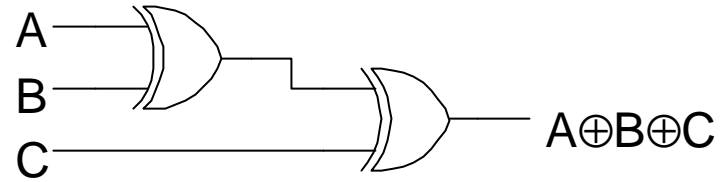

|||

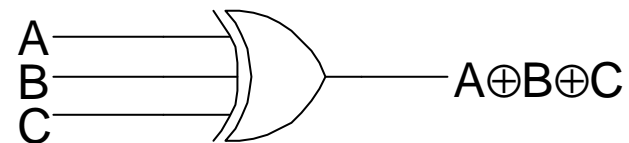

# IC Digital Logic Family

---

- RTL (Resistor Transistor Logic)
- DTL (Diode Transistor Logic)
- TTL (Transistor Transistor Logic) :
- ECL (Emitter Coupled Logic) :
- MOS (Metal Oxide Semiconductor) :
- CMOS (Complementary Metal Oxide Semiconductor) : ,
- I<sup>2</sup>L (Integrated Injection Logic) :



# Positive Logic and Negative Logic

❑ Positive logic ( )



❑ Negative logic ( )



**Positive logic  
AND**

X	Y	F
0	0	0
0	1	0
1	0	0
1	1	1

**Positive logic  
OR**

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	1

**Negative logic  
AND**

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	1

**Negative logic  
OR**

X	Y	F
0	0	0
0	1	0
1	0	0
1	1	1

❑ Positive logic AND = Negative logic OR

❑ Positive logic OR = Negative logic AND

# IC Logic Family

# 가

Fanout

,

(Power dissipation)

(Propagation delay)  
가

(Noise margin)