

## 4 Combinational Logic Circuit

---

4.1

4.2

4.3 가

4.4

4.5

4.6

4.7 NAND

4.8 NOR

4.9 XOR

# Combinational Logic Circuit

## □ Digital Logic Circuit

### ◆ Combinational logic circuit)


- $Y = f(X)$

- 

n

m

- No feedback

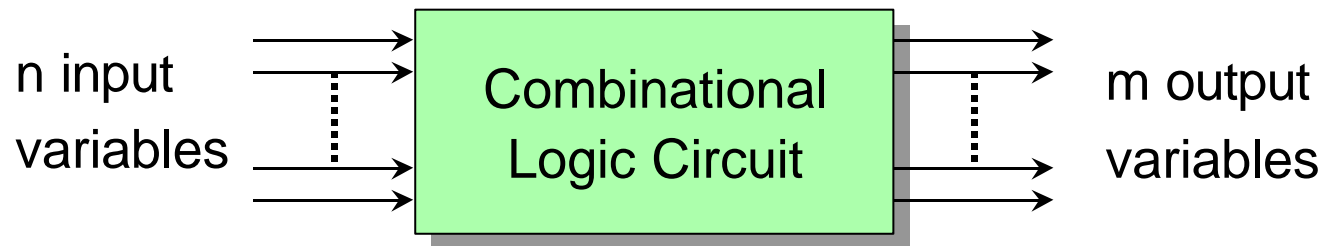

### ◆ Sequential logic circuit

- $Y = f(X, Y)$

- 

- feedback

# Design of Combinational Circuit

---


## □ Design Procedure

- (1)
- (2) Input, output variable
- (3) Input, output variable
- (4) Truth table -
- (5) Boolean function minimization
- (6) Logic diagram
- (7) Design verification



(fanout)

# Half-Adder

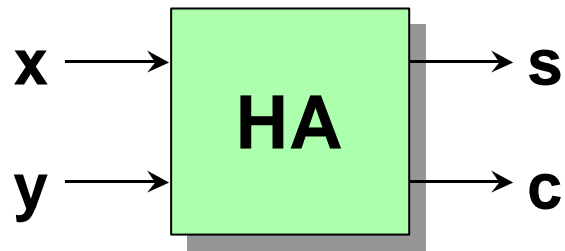


| x | y | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

A Karnaugh map for the Sum (S) output. The vertical axis is labeled 'x' with values 0 and 1. The horizontal axis is labeled 'y' with values 0 and 1. The map shows 1s in the cells (0,1) and (1,0), and 0s in the cells (0,0) and (1,1).





$$S = xy' + x'y$$
$$= x \dot{\wedge} y$$

A Karnaugh map for the Carry (C) output. The vertical axis is labeled 'x' with values 0 and 1. The horizontal axis is labeled 'y' with values 0 and 1. The map shows a 1 in the cell (1,1) and 0s in the cells (0,0), (0,1), and (1,0).


$$C = xy$$

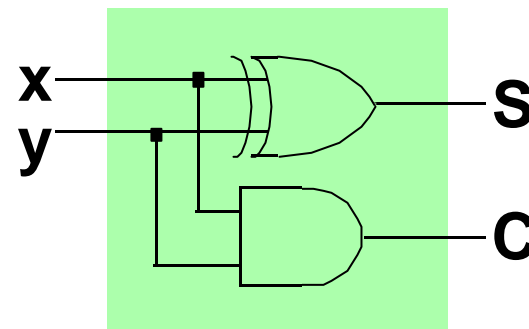

# Half-Adder

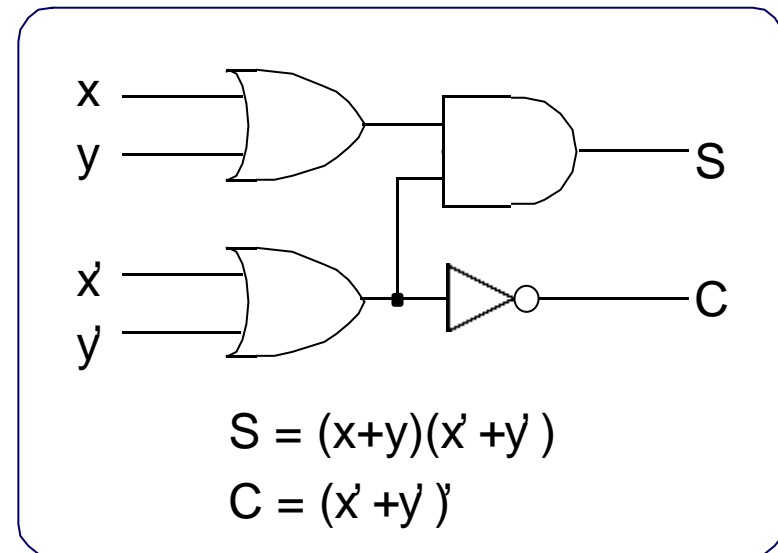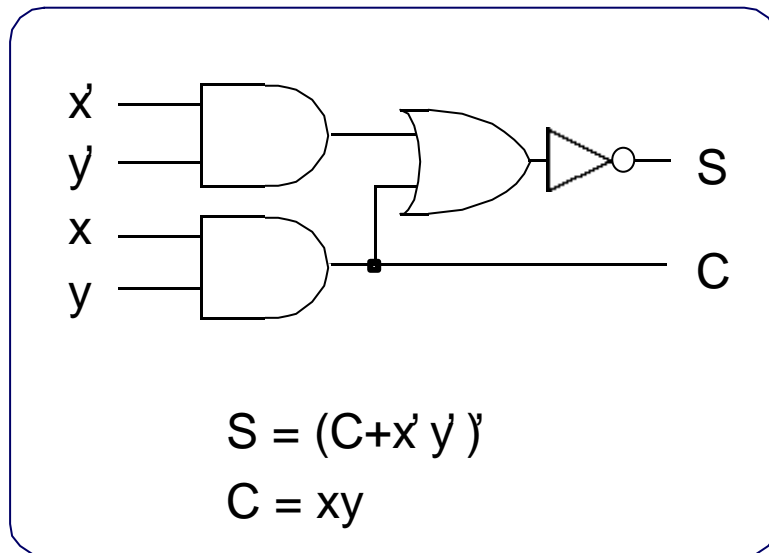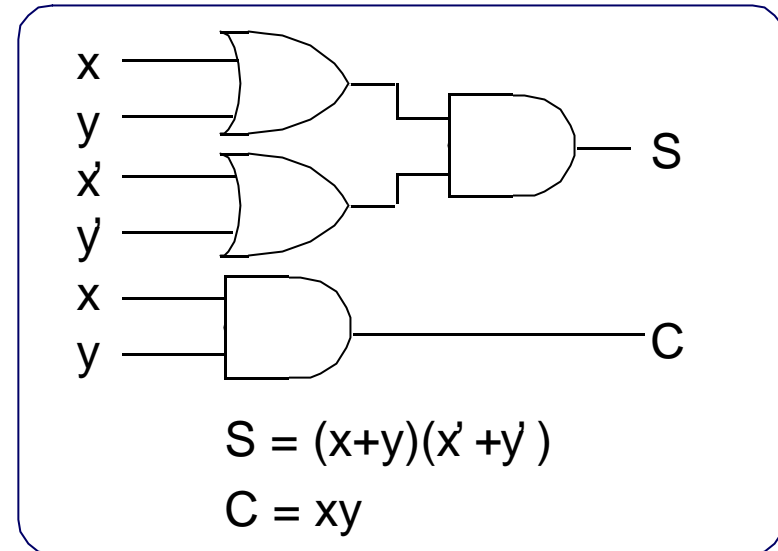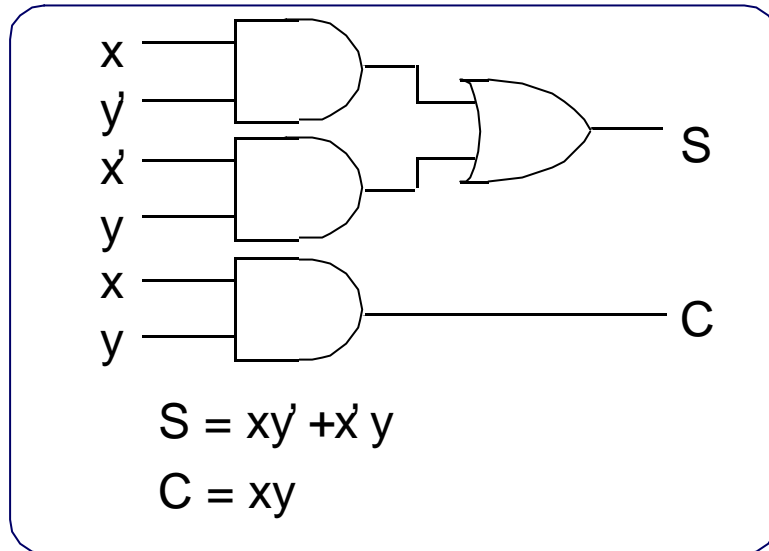

# Full-Adder

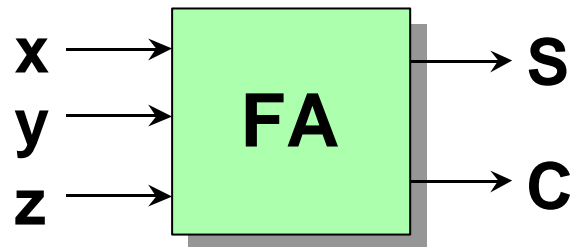

| x | y | z | S | C |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    | 1  |    | 1  |
| 1      | 1  |    | 1  |    |

$$\begin{aligned}
 S &= xy'z' + x'y'z + x'yz' + xyz \\
 &= x'(y'z + yz') + x(yz + y'z') \\
 &= x'(y \oplus z) + x(y \oplus z)' \\
 &= x \oplus y \oplus z
 \end{aligned}$$

| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    |    | 1  |    |
| 1      |    | 1  | 1  | 1  |

$$C = xy + yz + xz$$

| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    |    | 1  |    |
| 1      |    | 1  | 1  | 1  |

$$\begin{aligned}
 C &= xy + x'yz + xy'z \\
 &= xy + z(x'y + xy') \\
 &= xy + z(x \oplus y)
 \end{aligned}$$



# Full-Adder

$$S = xy'z' + x'y'z + x'yz' + xyz$$


$$C = xy + yz + xz$$

$$S = x \oplus y \oplus z$$

$$C = xy + z(x \oplus y)$$

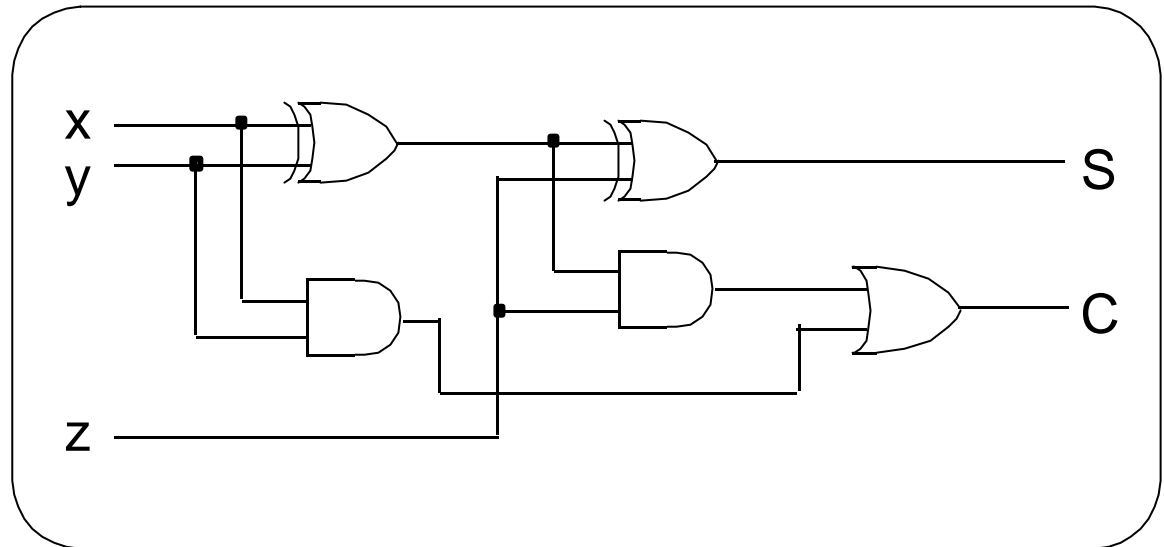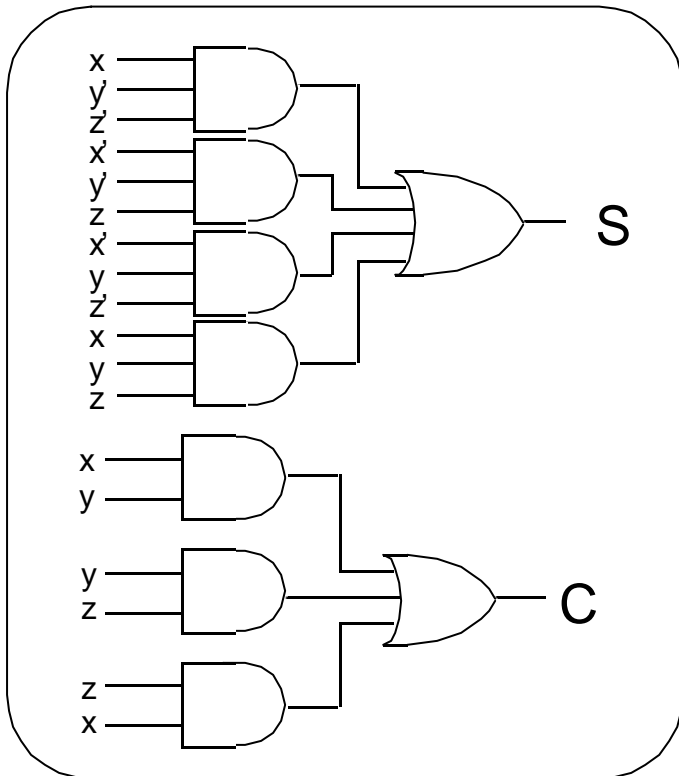

# Half-Subtractor

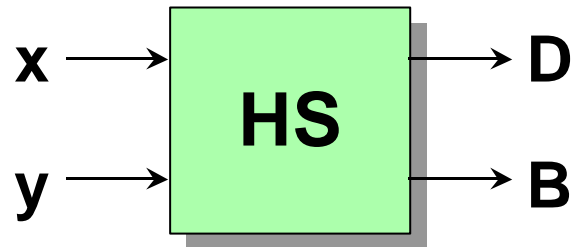


| x | y | D | B |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

| x \ y | 0 | 1 |
|-------|---|---|
| 0     |   | 1 |
| 1     | 1 |   |

| x \ y | 0 | 1 |
|-------|---|---|
| 0     |   | 1 |
| 1     |   |   |


$$D = xy' + x'y$$
$$= x \dot{\wedge} y$$

$$B = x'y$$

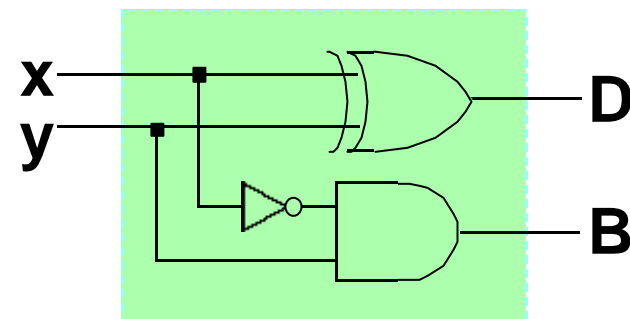



# Full-Subtractor

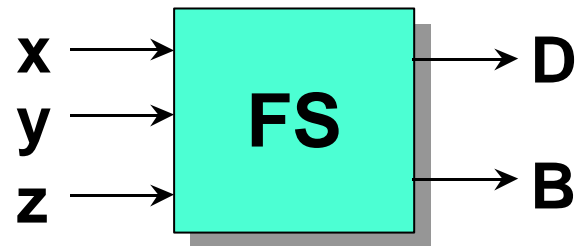

| x | y | z | D | B |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    | 1  |    | 1  |
| 1      | 1  |    | 1  |    |

$$\begin{aligned}
 D &= xy'z' + x'y'z + x'yz' + xyz \\
 &= x'(y'z + yz') + x(yz + y'z') \\
 &= x'(y \oplus z) + x(y \oplus z)' \\
 &= x \oplus y \oplus z
 \end{aligned}$$

| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    | 1  | 1  | 1  |
| 1      |    |    | 1  |    |

$$B = x'y + yz + x'z$$



| x \ yz | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    | 1  | 1  | 1  |
| 1      |    |    | 1  |    |

$$\begin{aligned}
 B &= x'y + xyz + x'y'z \\
 &= x'y + z(xy + x'y') \\
 &= x'y + z(x \oplus y)'
 \end{aligned}$$

# Full-subtractor

$$D = x \oplus y \oplus z$$

$$B = x' y + z(x \oplus y)'$$

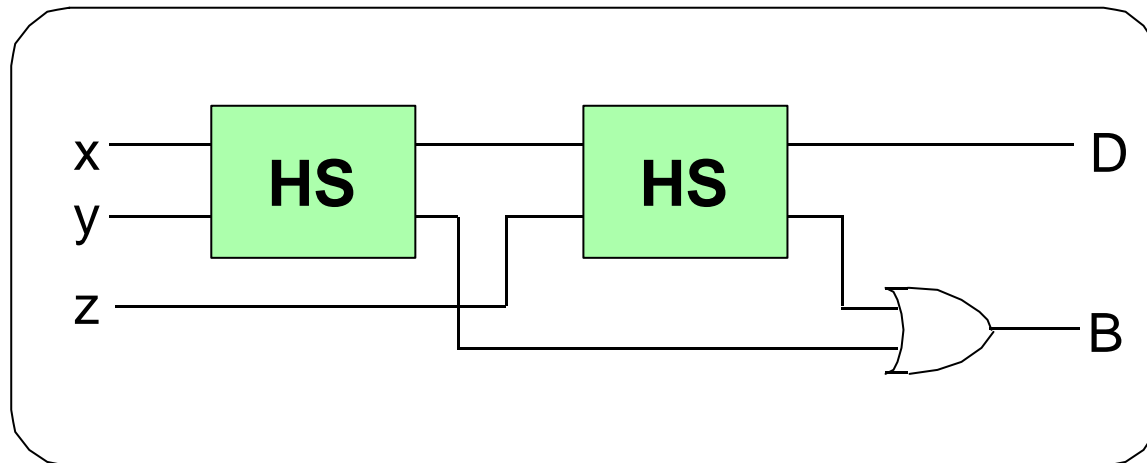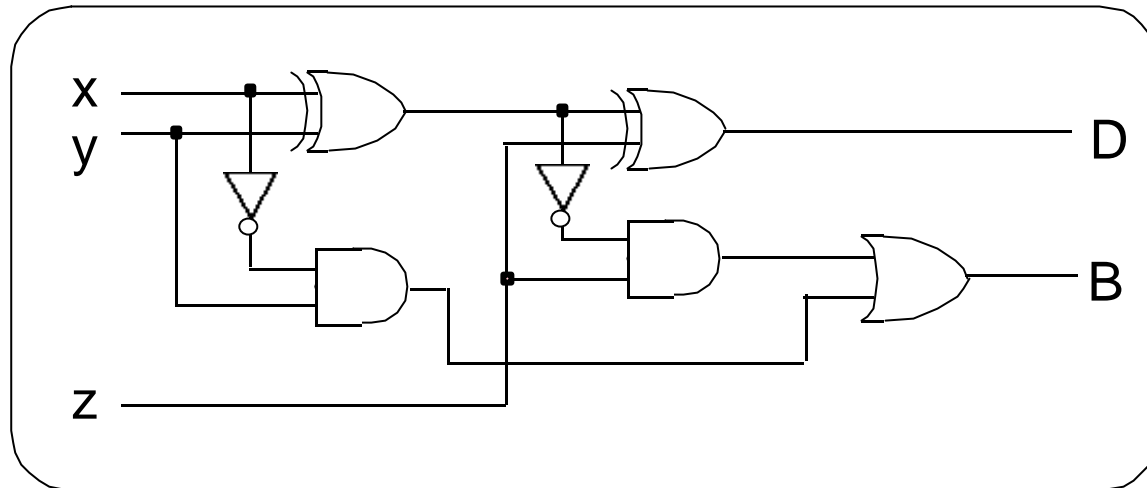

# BCD to Excess-3 Code Converter

| A | B | C | D | w | x | y | z |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |

$$w(A,B,C,D) = \sum(5,6,7,8,9)$$

$$x(A,B,C,D) = \sum(1,2,3,4,9)$$

$$y(A,B,C,D) = \sum(0,3,4,7,8)$$

$$z(A,B,C,D) = \sum(0,2,4,6,8)$$

$$d(A,B,C,D) = \sum(10,11,12,13,14,15)$$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    |    |    |    |
| 01      |    | 1  | 1  | 1  |
| 11      | X  | X  | X  | X  |
| 10      | 1  | 1  | X  | X  |

$$w = A + BC + BD$$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    | 1  | 1  | 1  |
| 01      | 1  |    |    |    |
| 11      | X  | X  | X  | X  |
| 10      |    | 1  | X  | X  |

$$x = B' C + B' D + BC' D'$$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  |    | 1  |    |
| 01      | 1  |    | 1  |    |
| 11      | X  | X  | X  | X  |
| 10      | 1  |    | X  | X  |

$$y = CD + C' D'$$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  |    |    | 1  |
| 01      | 1  |    |    | 1  |
| 11      | X  | X  | X  | X  |
| 10      | 1  |    | X  | X  |

$$z = D'$$

## BCD to Excess-3 Code Converter



$$w = A + BC + BD$$

$$= A + B(C + D)$$

$$x = B' C + B' D + BC' D'$$


$$= B' (C + D) + BC' D'$$

$$= B' (C + D) + B(C + D)'$$

$$y = CD + C' D'$$

$$= CD + (C + D)'$$



$$z = D'$$

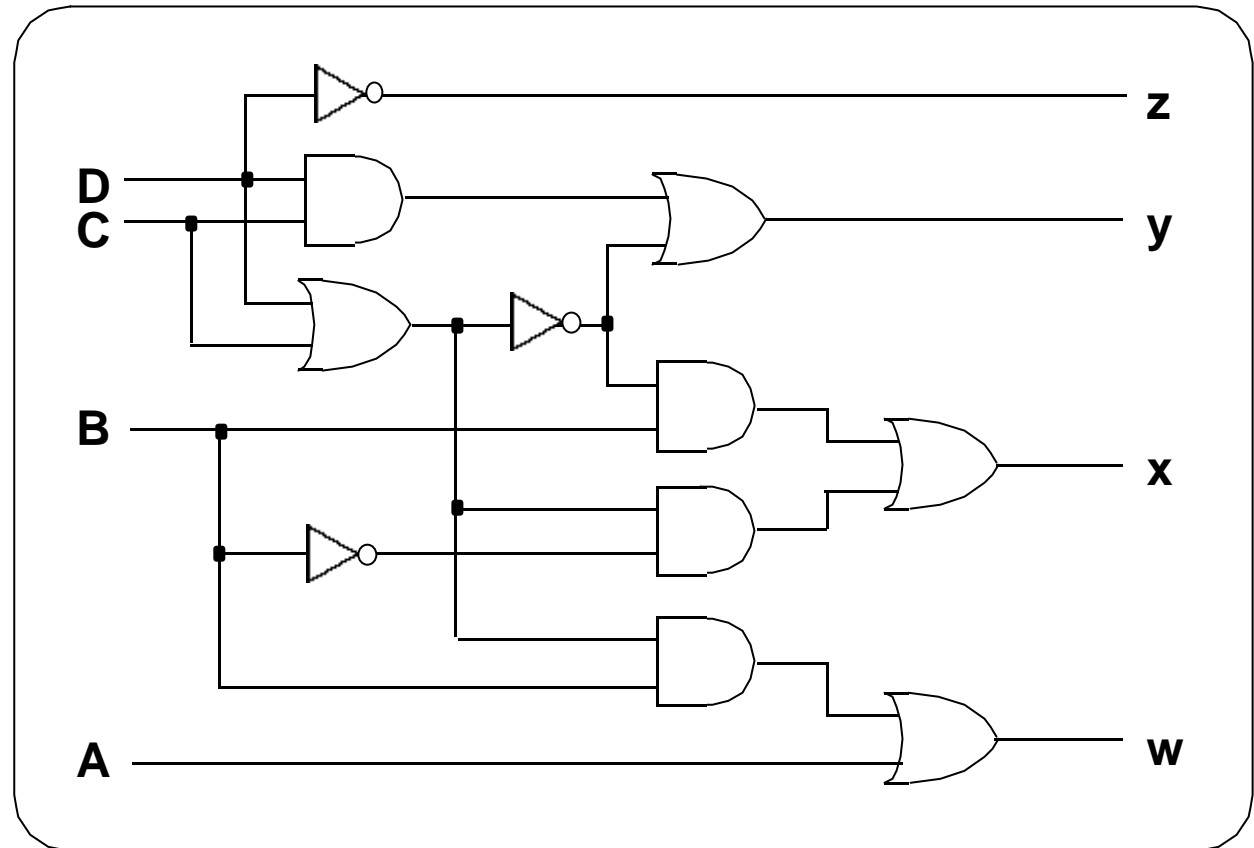

: AND(7), OR(3)

: AND(4), OR(4)

# BCD to 7-Segment Display

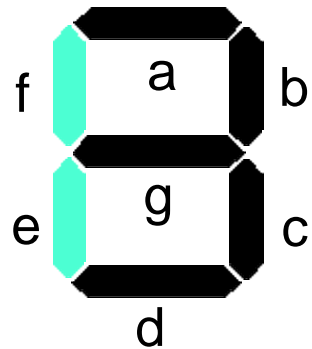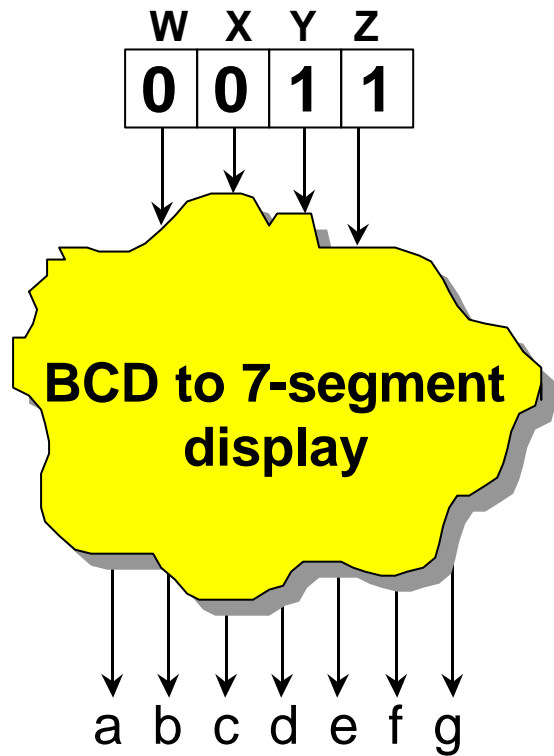

| W | X | Y | Z | a | b | c | d | e | f | g |
|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 0 | 0 | 0 | 1 |   |   |   |   |   |   |   |
| 0 | 0 | 1 | 0 |   |   |   |   |   |   |   |
| 0 | 0 | 1 | 1 |   |   |   |   |   |   |   |
| 0 | 1 | 0 | 0 |   |   |   |   |   |   |   |
| 0 | 1 | 0 | 1 |   |   |   |   |   |   |   |
| 0 | 1 | 1 | 0 |   |   |   |   |   |   |   |
| 0 | 1 | 1 | 1 |   |   |   |   |   |   |   |
| 1 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 1 | 0 | 0 | 1 |   |   |   |   |   |   |   |
| 1 | 0 | 1 | 0 |   |   |   |   |   |   |   |
| 1 | 0 | 1 | 1 |   |   |   |   |   |   |   |
| 1 | 1 | 0 | 0 |   |   |   |   |   |   |   |
| 1 | 1 | 0 | 1 |   |   |   |   |   |   |   |
| 1 | 1 | 1 | 0 |   |   |   |   |   |   |   |
| 1 | 1 | 1 | 1 |   |   |   |   |   |   |   |

# BCD to 7-Segment Display

---

**W** →

**X** →

**Y** →

**Z** →

→ **a**

→ **b**

→ **c**

→ **d**

→ **e**


→ **f**

→ **g**

# Analysis of Combinational Circuit

(1)

- 
- 
- 
- 

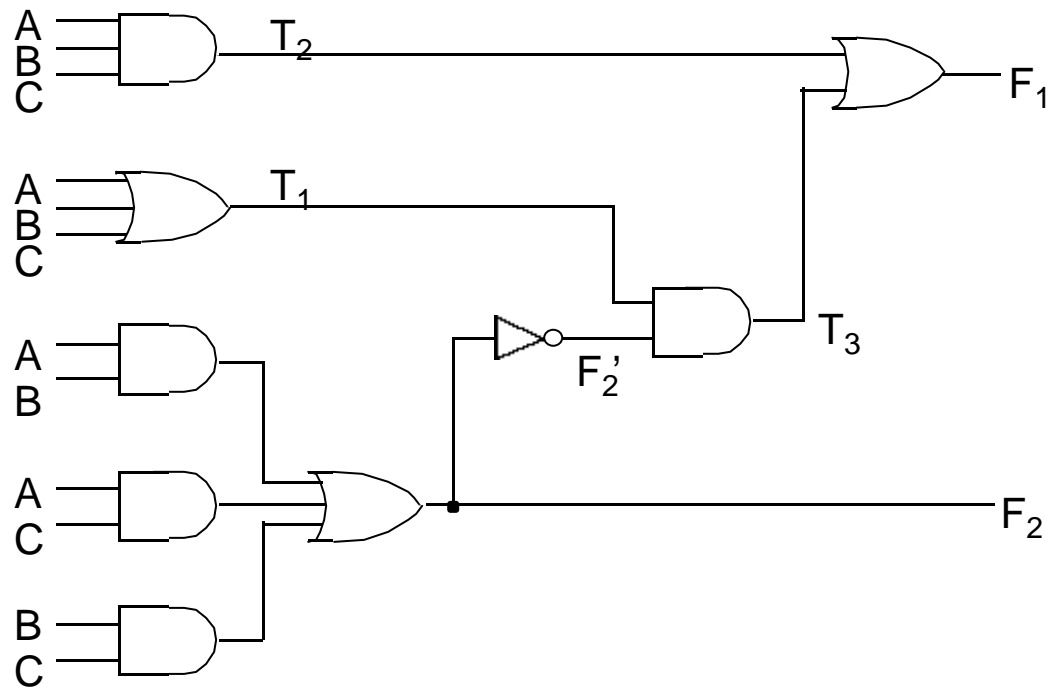

$$F_2 = AB + BC + CA$$

$$T_1 = A + B + C$$

$$T_2 = ABC$$

$$T_3 = F_2' T_1$$

$$F_1 = T_2 + T_3$$

$$F_1 = T_2 + T_3$$

$$= ABC + F_2' T_1$$

$$= ABC + (AB + BC + CA)' (A + B + C)$$


$$= A' BC + A' B' C + AB' C + ABC$$

$$= A \oplus B \oplus C$$

# Analysis of Combinational Circuit

(2)

map

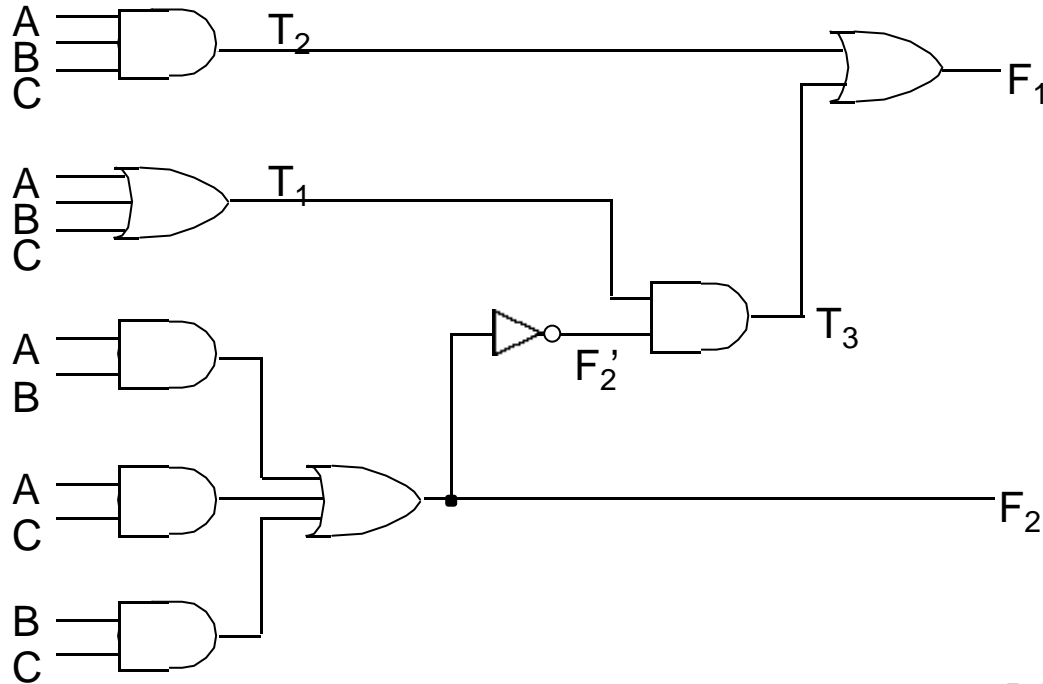

| A | B | C | $F_2$ | $F_2'$ | $T_1$ | $T_2$ | $T_3$ | $F_1$ |
|---|---|---|-------|--------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0     | 1      | 0     | 0     | 0     | 0     |
| 0 | 0 | 1 | 0     | 1      | 1     | 0     | 1     | 0     |
| 0 | 1 | 0 | 0     | 1      | 1     | 0     | 1     | 0     |
| 0 | 1 | 1 | 1     | 0      | 1     | 0     | 0     | 1     |
| 1 | 0 | 0 | 0     | 1      | 1     | 0     | 1     | 0     |
| 1 | 0 | 1 | 1     | 0      | 1     | 0     | 0     | 1     |
| 1 | 1 | 0 | 1     | 0      | 1     | 0     | 0     | 1     |
| 1 | 1 | 1 | 1     | 0      | 1     | 1     | 0     | 1     |

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    | 1  |    | 1  |
| 1      | 1  |    | 1  |    |

$$F_1 = A \oplus B \oplus C$$

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    |    | 1  |    |
| 1      |    | 1  | 1  | 1  |


$$F_2 = AB + BC + CA$$




# Multi-Level NAND Circuit

---



**NOT**

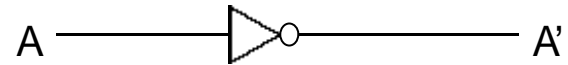







**AND**

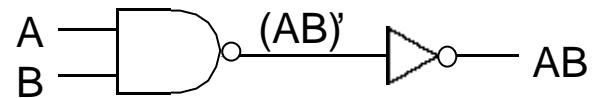

**OR**

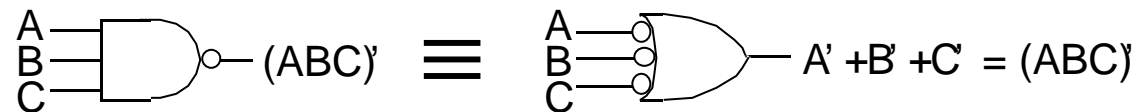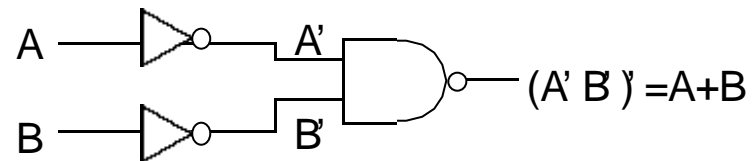


# Multi-Level NAND Circuit

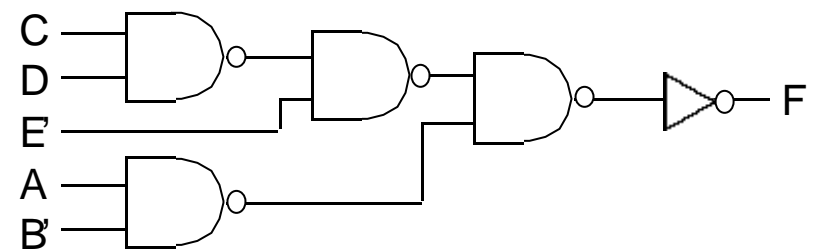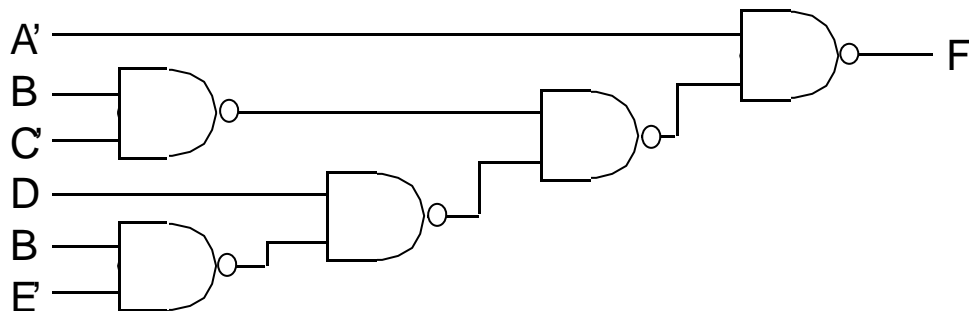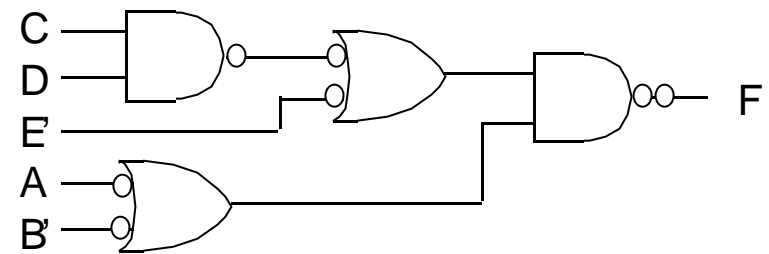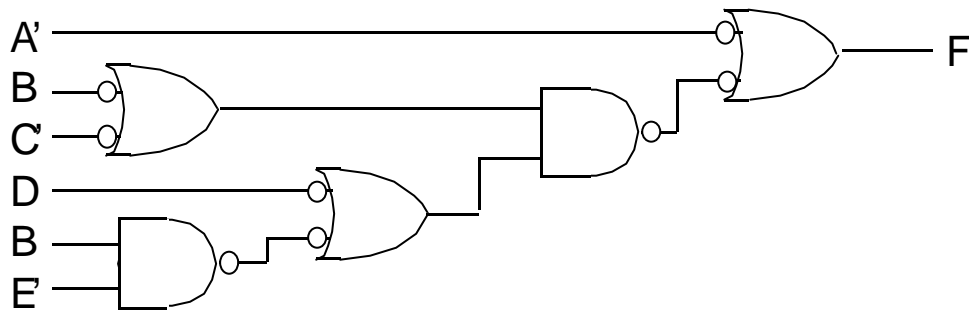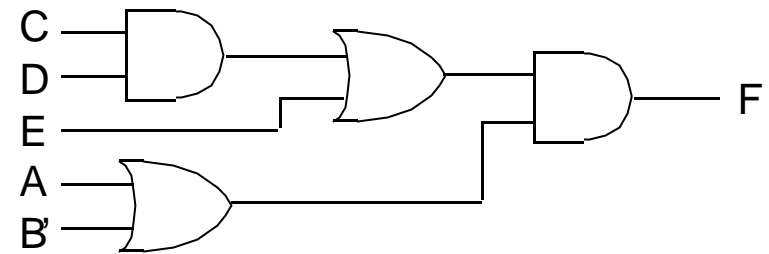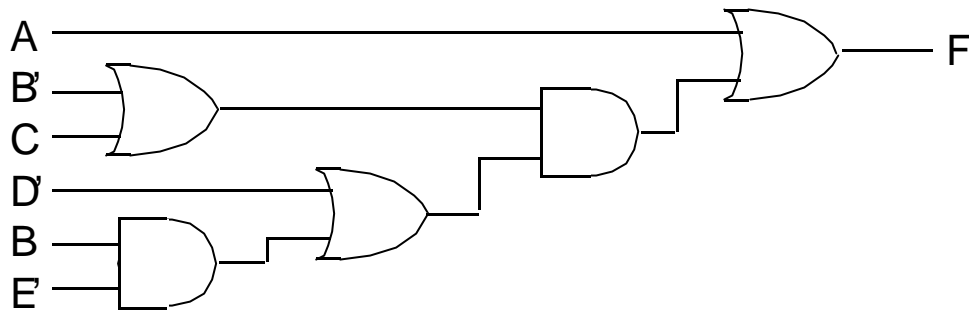

# Analysis of Multi-Level NAND Circuit

(1)

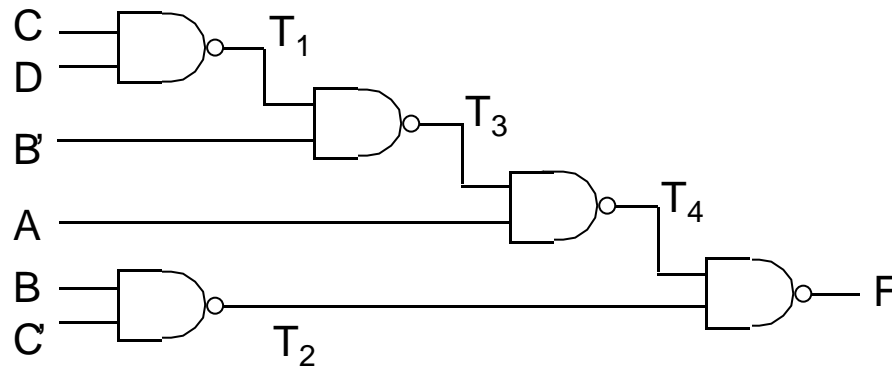

$$T_1 = (CD)' = C + D'$$

$$T_2 = (BC')' = B + C$$

$$T_3 = (T_1 B')' = [(C + D)B'] = (B'C + B'D)'$$

$$= (B + C)(B + D) = B + CD$$


$$T_4 = (AT_3)' = [A(B + CD)]$$

$$F = (T_2 T_4)' = (BC')[A(B + CD)]$$

$$= BC + A(B + CD)$$

# Analysis of Multi-Level NAND Circuit

(2) Truth table          map

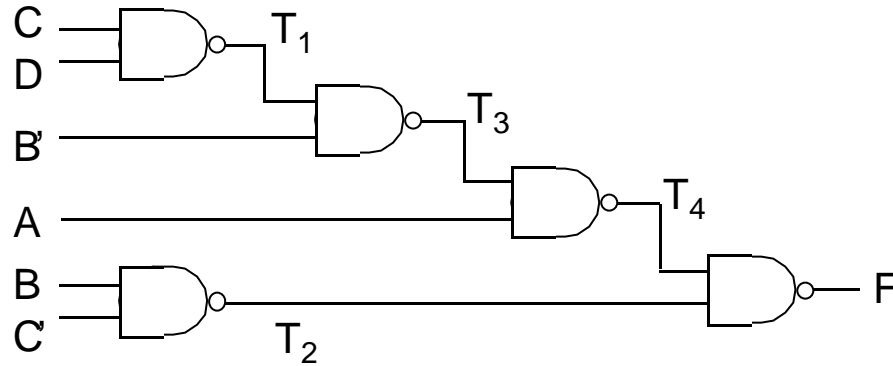

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | CD |    |    |    |
|    |    | 00 | 01 | 11 | 10 |
| AB | 00 |    |    |    |    |
|    | 01 | 1  | 1  |    |    |
|    | 11 | 1  | 1  | 1  | 1  |
|    | 10 |    |    | 1  |    |




$$F = AB + BC' + ACD$$

$$= A(B + CD) + BC'$$

| A | B | C | D | T <sub>1</sub> | T <sub>2</sub> | T <sub>3</sub> | T <sub>4</sub> | F |
|---|---|---|---|----------------|----------------|----------------|----------------|---|
| 0 | 0 | 0 | 0 | 1              | 1              | 0              | 0              | 0 |
| 0 | 0 | 0 | 1 | 1              | 1              | 0              | 0              | 0 |
| 0 | 0 | 1 | 0 | 1              | 1              | 0              | 0              | 0 |
| 0 | 0 | 1 | 1 | 0              | 1              | 1              | 1              | 0 |
| 0 | 1 | 0 | 0 | 1              | 0              | 1              | 1              | 1 |
| 0 | 1 | 0 | 1 | 1              | 0              | 1              | 1              | 1 |
| 0 | 1 | 1 | 0 | 1              | 1              | 1              | 1              | 0 |
| 0 | 1 | 1 | 1 | 0              | 1              | 1              | 1              | 0 |
| 1 | 0 | 0 | 0 | 1              | 1              | 0              | 0              | 0 |
| 1 | 0 | 0 | 1 | 1              | 1              | 0              | 0              | 0 |
| 1 | 0 | 1 | 0 | 1              | 1              | 0              | 0              | 0 |
| 1 | 0 | 1 | 1 | 0              | 1              | 1              | 1              | 1 |
| 1 | 1 | 0 | 0 | 1              | 0              | 1              | 1              | 1 |
| 1 | 1 | 0 | 1 | 1              | 0              | 1              | 1              | 1 |
| 1 | 1 | 1 | 0 | 1              | 1              | 1              | 1              | 1 |
| 1 | 1 | 1 | 1 | 0              | 1              | 1              | 1              | 1 |

# Analysis of Multi-Level NAND Circuit

## (3) AND-OR

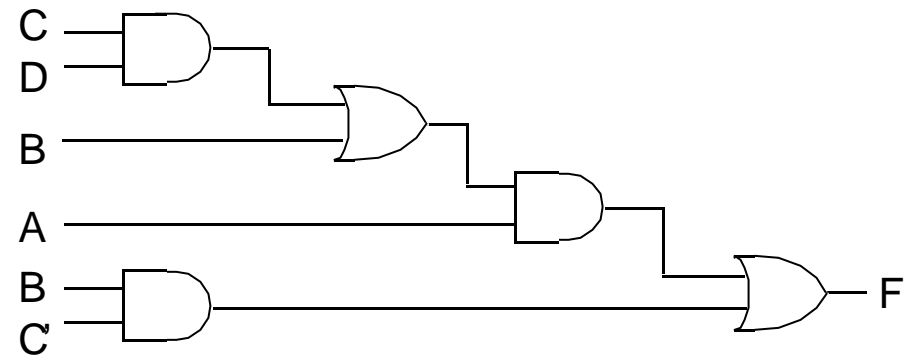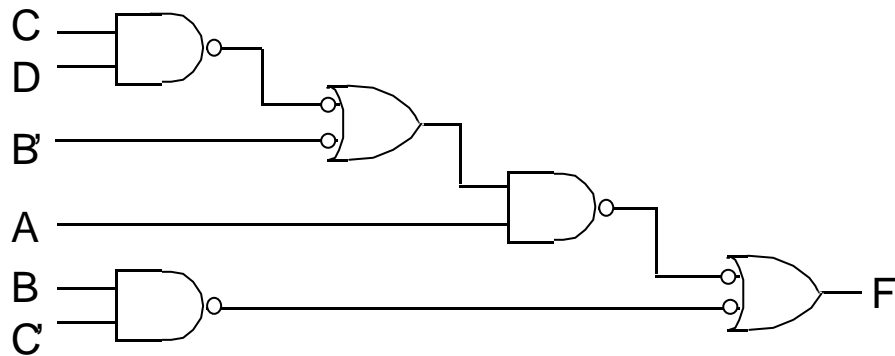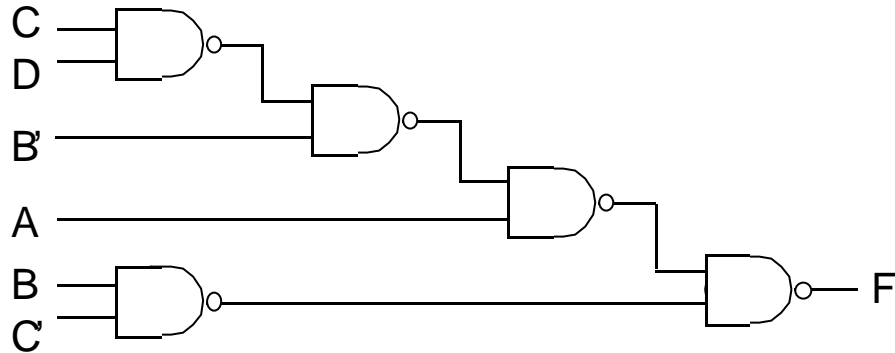


$$F = A(B+CD)+BC'$$


# Multi-Level NOR Circuit

---



**NOT**

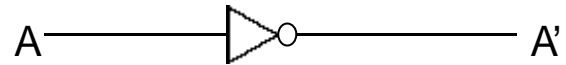




**AND**

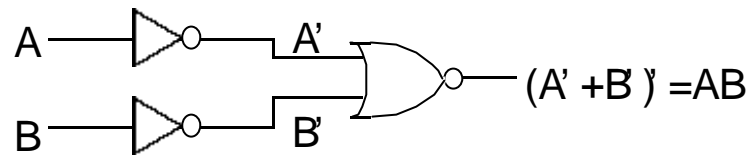




**OR**

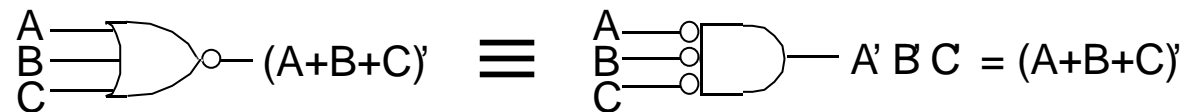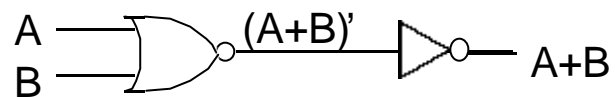

## Multi-Level NOR Circuit

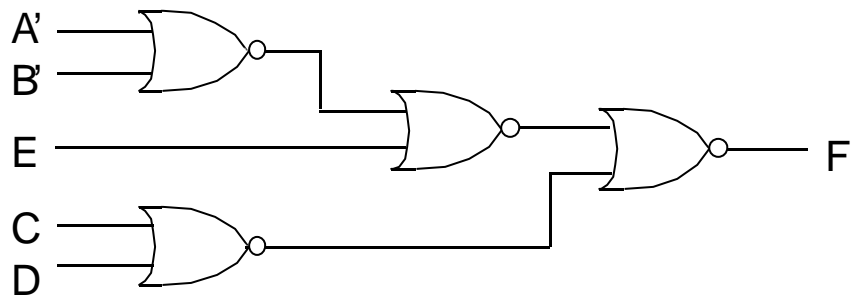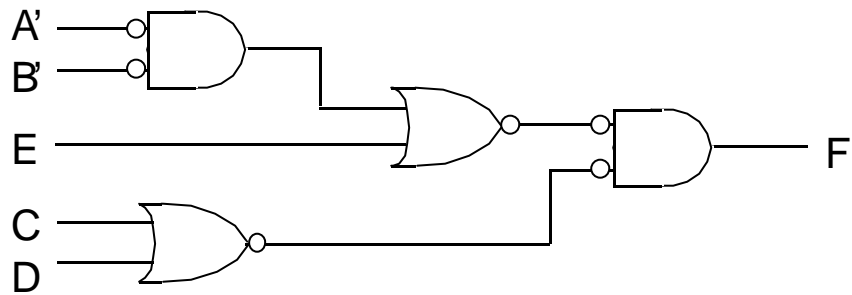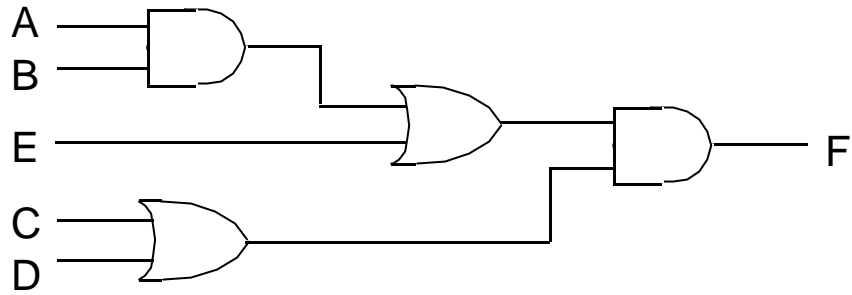

## Multi-Level NOR Circuit

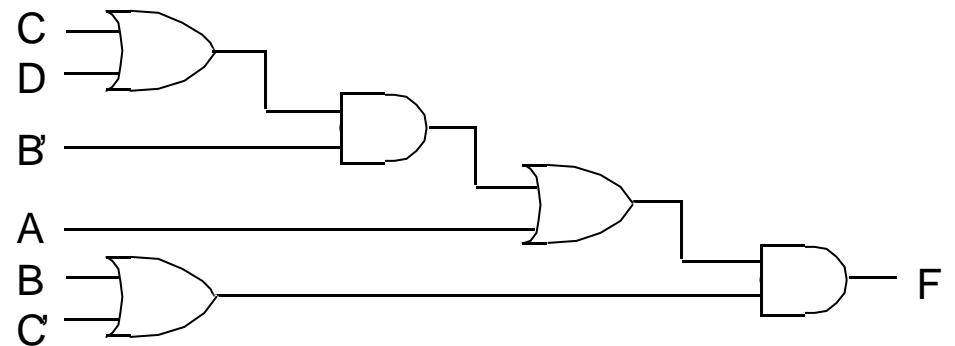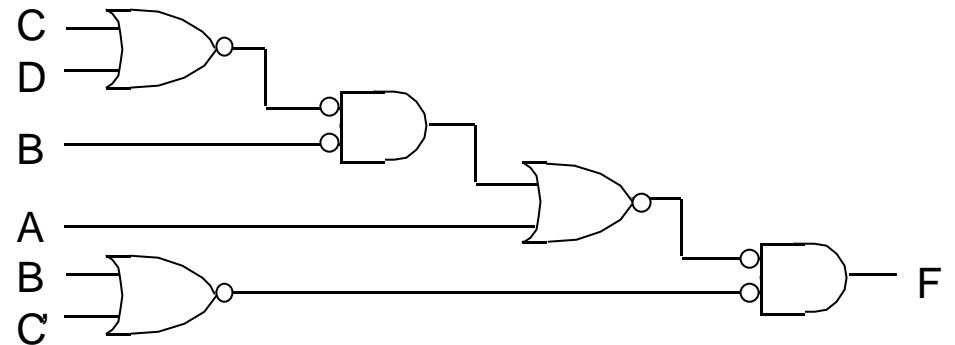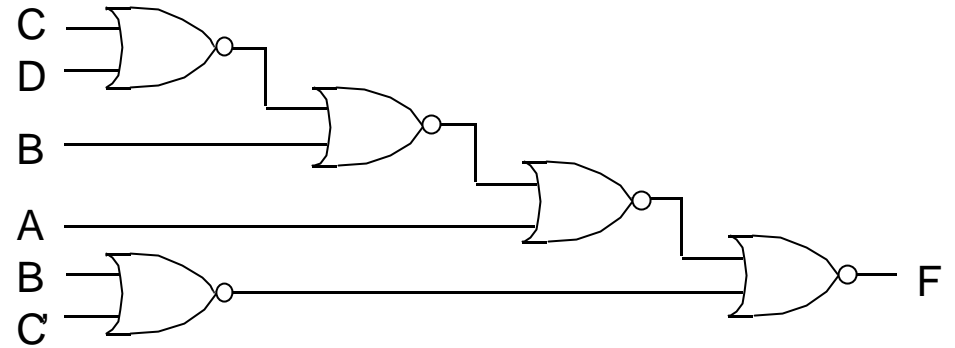

## XOR function

$$x \oplus y = x' y + x y'$$

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$



$$x \oplus x' = 1$$

$$x \oplus y' = (x \oplus y)' = x y$$

$$x' \oplus y = (x \oplus y)' = x y$$

$$x y' = (x \oplus y)' = x \oplus y$$

$$x' y = (x \oplus y)' = x \oplus y$$

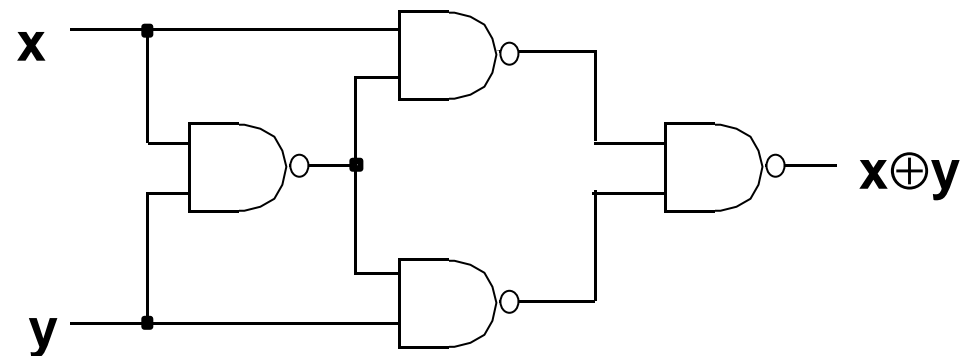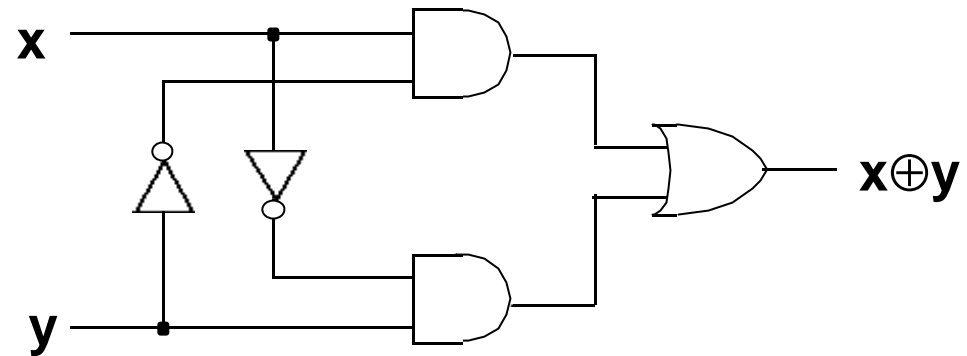





# Odd function

# Even function

“1” 가 “1”

|   |    |    |    |    |
|---|----|----|----|----|
|   | BC |    |    |    |
| A | 00 | 01 | 11 | 10 |
| 0 |    | 1  |    | 1  |
| 1 | 1  |    | 1  |    |


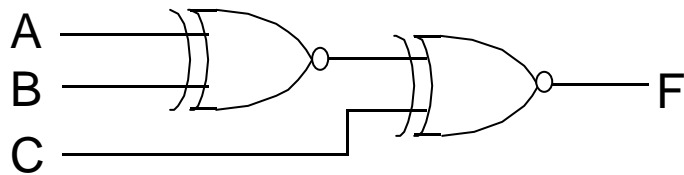
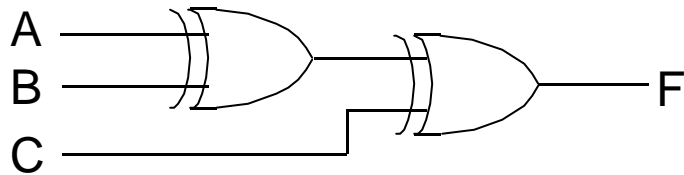
$$\begin{aligned}
 F &= A \oplus B \oplus C \\
 &= A \oplus (B \oplus C) \\
 &= A \oplus B \oplus C
 \end{aligned}$$



“1” 가 “1”

|   |    |    |    |    |
|---|----|----|----|----|
|   | BC |    |    |    |
| A | 00 | 01 | 11 | 10 |
| 0 | 1  |    | 1  |    |
| 1 |    | 1  |    | 1  |
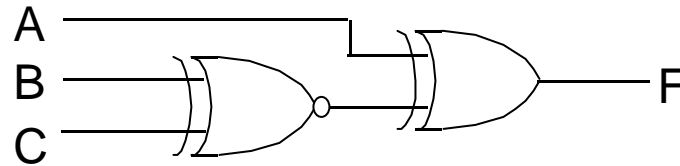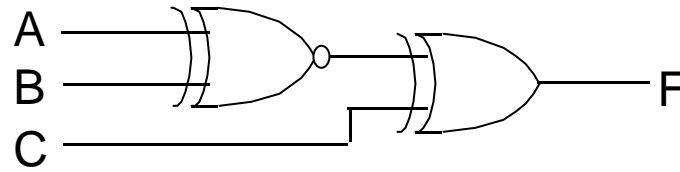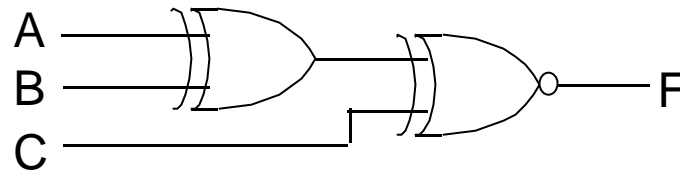
$$\begin{aligned}
 F &= (A \oplus B \oplus C)' \\
 &= A \oplus (B \oplus C)' = A \oplus (B \oplus C) \\
 &= (A \oplus B)' \oplus C = (A \oplus B) \oplus C
 \end{aligned}$$




# Parity Generator

| x | y | z | $P_{\text{odd}}$ | $P_{\text{even}}$ |
|---|---|---|------------------|-------------------|
| 0 | 0 | 0 | 1                | 0                 |
| 0 | 0 | 1 | 0                | 1                 |
| 0 | 0 | 0 | 0                | 1                 |
| 0 | 1 | 1 | 1                | 0                 |
| 1 | 1 | 0 | 0                | 1                 |
| 1 | 0 | 1 | 1                | 0                 |
| 1 | 0 | 0 | 1                | 0                 |
| 1 | 1 | 1 | 0                | 1                 |

## Odd parity

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 1  |    | 1  |    |
| 1      |    | 1  |    | 1  |

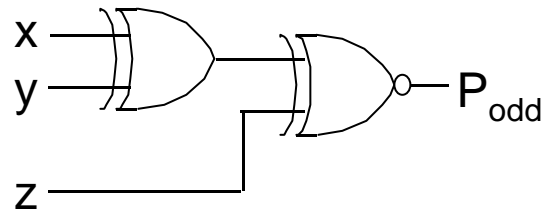
$$\begin{aligned}
 P_{\text{odd}} &= (x \oplus y \oplus z)' \\
 &= x \oplus (y \oplus z) \\
 &= (x \oplus y) \oplus z
 \end{aligned}$$



## Even parity

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      |    | 1  |    | 1  |
| 1      | 1  |    | 1  |    |
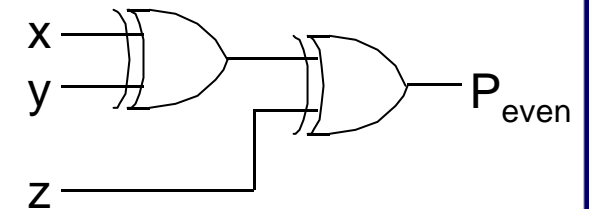
$$\begin{aligned}
 P_{\text{even}} &= x \oplus y \oplus z \\
 &= [x \oplus y \oplus z]' \\
 &= [x \oplus (y \oplus z)] \\
 &= x \oplus y \oplus z
 \end{aligned}$$



(cf)  $(x \oplus y) \oplus z = x \oplus (y \oplus z)$

# Parity Checker

| x | y | z | P | $C_{\text{odd}}$ | $C_{\text{even}}$ |
|---|---|---|---|------------------|-------------------|
| 0 | 0 | 0 | 0 | 1                | 0                 |
| 0 | 0 | 0 | 1 | 0                | 1                 |
| 0 | 0 | 1 | 0 | 0                | 1                 |
| 0 | 0 | 1 | 1 | 1                | 0                 |
| 0 | 1 | 0 | 0 | 0                | 1                 |
| 0 | 1 | 0 | 1 | 1                | 0                 |
| 0 | 1 | 1 | 0 | 1                | 0                 |
| 0 | 1 | 1 | 1 | 0                | 1                 |
| 1 | 0 | 0 | 0 | 0                | 1                 |
| 1 | 0 | 0 | 1 | 1                | 0                 |
| 1 | 0 | 1 | 0 | 1                | 0                 |
| 1 | 0 | 1 | 1 | 0                | 1                 |
| 1 | 1 | 0 | 0 | 1                | 0                 |
| 1 | 1 | 0 | 1 | 0                | 1                 |
| 1 | 1 | 1 | 0 | 0                | 1                 |
| 1 | 1 | 1 | 1 | 1                | 0                 |

## Odd parity

| xy \ zP | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  |    | 1  |    |
| 01      |    | 1  |    | 1  |
| 11      | 1  |    | 1  |    |
| 10      |    | 1  |    | 1  |

$$\begin{aligned}
 C_{\text{odd}} &= (x \oplus y \oplus z \oplus P)' \\
 &= x (y \oplus z \oplus P)' \\
 &= x y (z \oplus P)' \\
 &= x y z P
 \end{aligned}$$

## Even parity

| xy \ zP | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    | 1  |    | 1  |
| 01      | 1  |    | 1  |    |
| 11      |    | 1  |    | 1  |
| 10      | 1  |    | 1  |    |

$$C_{\text{even}} = x \oplus y \oplus z \oplus P$$