
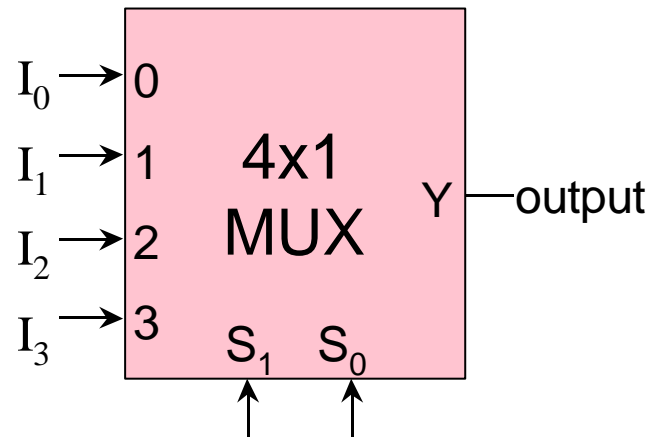


Multiplexer(MUX) or Data Selector

-
- 4x1 multiplexer

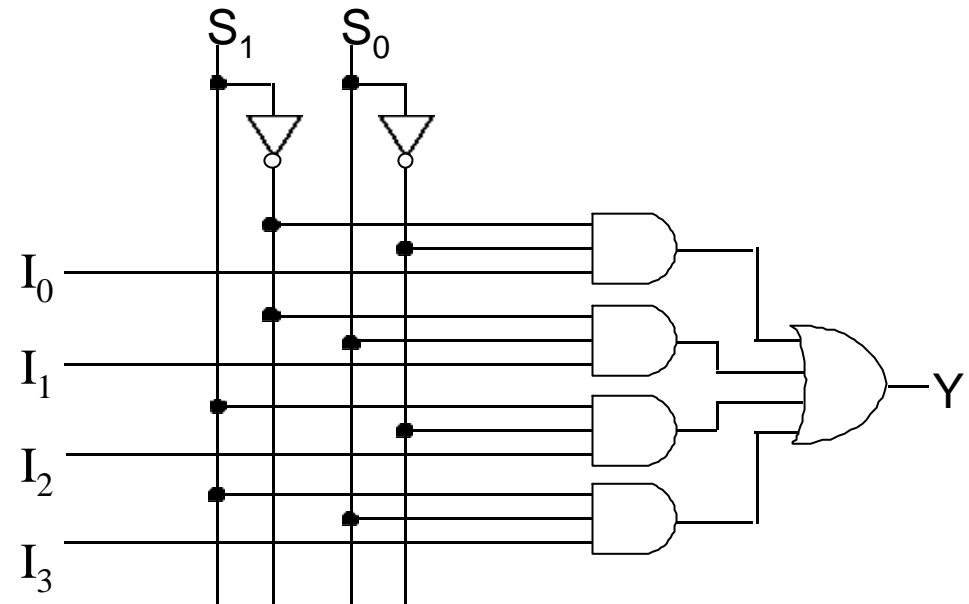

selector		output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3






Multiplexer

□ 2x1 MUX : $Y = S_0' I_0 + S_0 I_1$


□ 4x1 MUX : $Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$

□ 8x1 MUX : $Y = S_2' S_1' S_0' I_0 + S_2' S_1' S_0 I_1 + S_2' S_1 S_0' I_2 + S_2' S_1 S_0 I_3 + \dots$

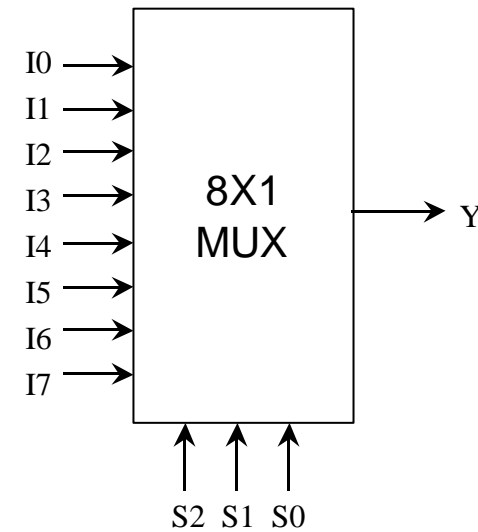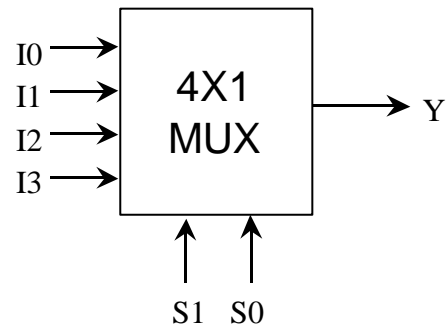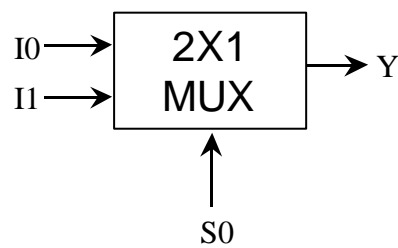


Quadruple 2-to-1 Line Multiplexer


□ 4bit A, B 4bit

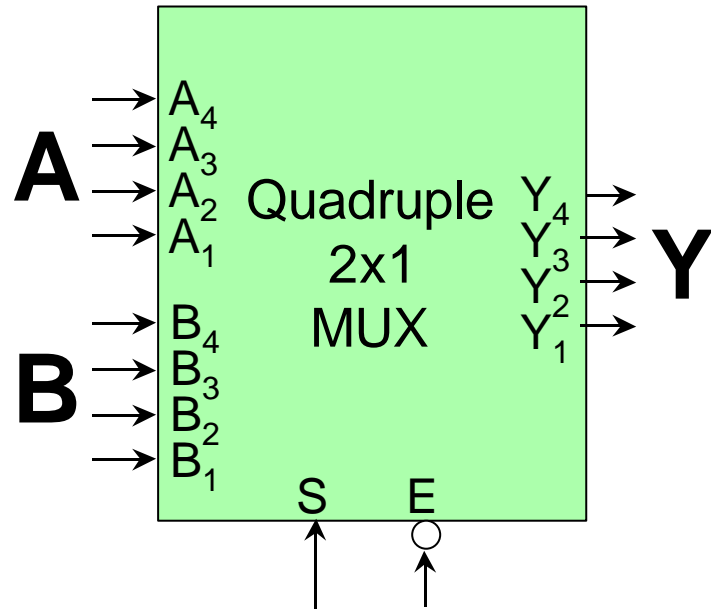

E	S	Y
1	X	all 0
0	0	A
0	1	B

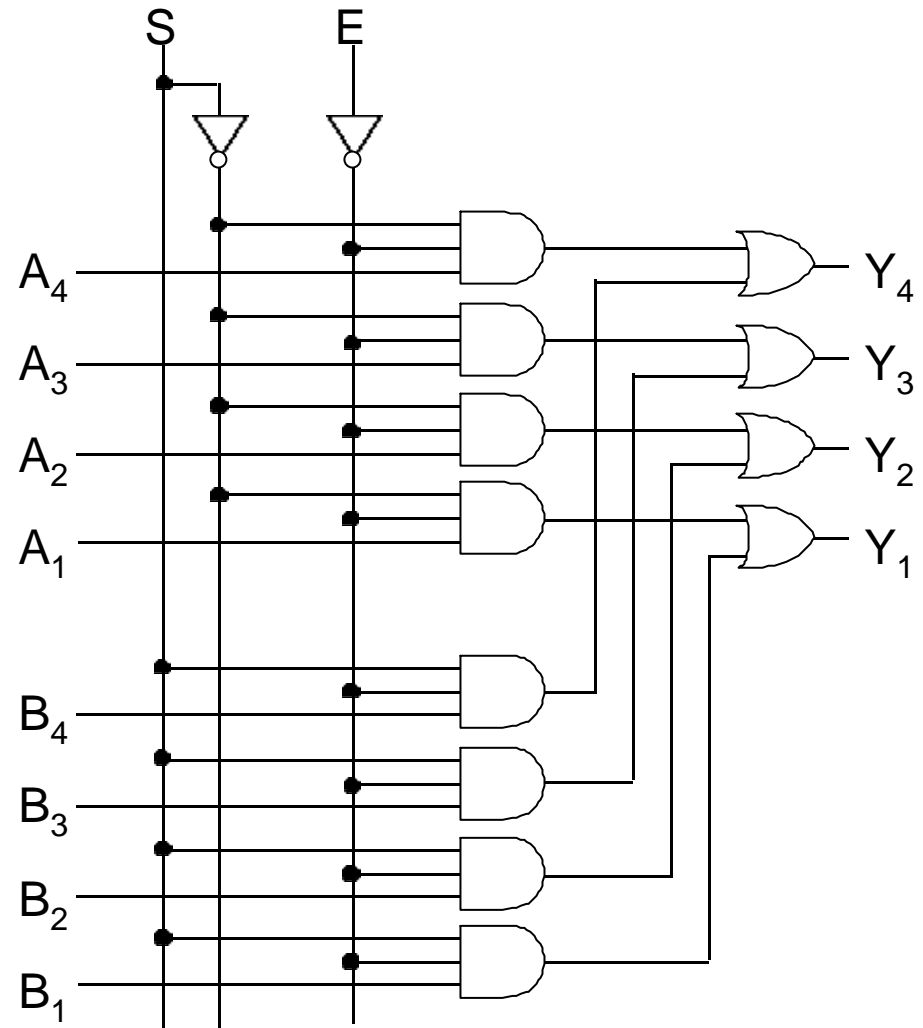

4x1 Multiplexer with Transmission Gate

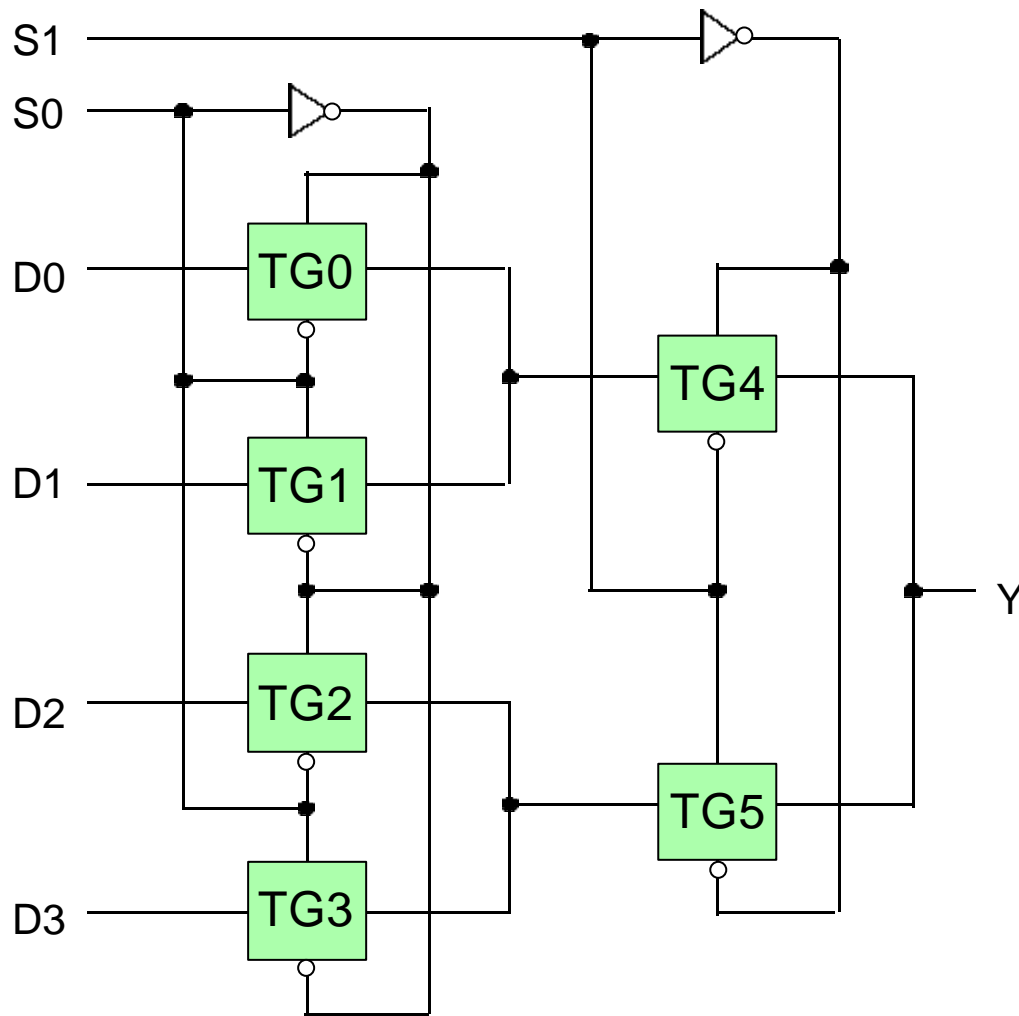

		ON
S0	0	0,2
	1	1,3
S1	0	4
	1	5



S1 S0	0 0	0 1	1 0	1 1
1 st level	0,2	1,3	0,2	1,3
2 nd level	4	4	5	5
Y	D0	D1	D2	D3

8x1 Multiplexer with Transmission Gate

8x1 MUX

Cascading Multiplexer

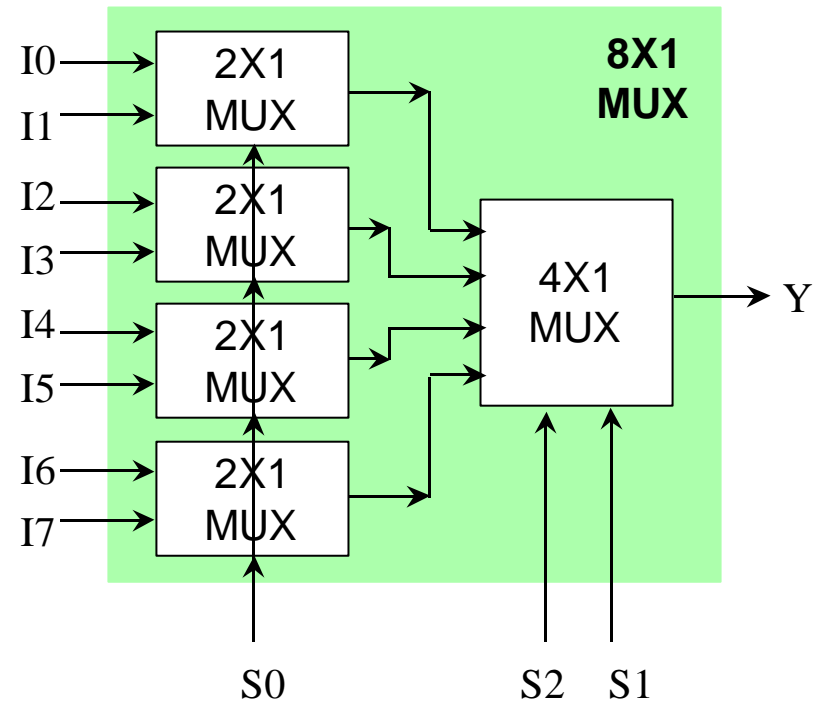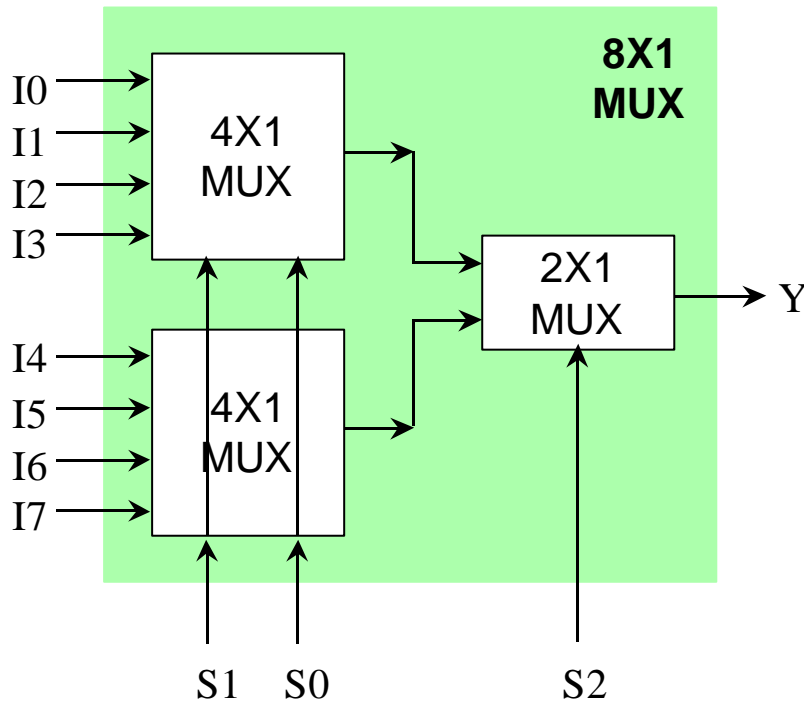- Large multiplexers can be formed from smaller ones



Multiplexer

Bool

() $F(A,B,C) = \Sigma(1,3,5,6)$


minterm	A	B	C	F
m_0	0	0	0	0
m_1	0	0	1	1
m_2	0	1	0	0
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	1
m_7	1	1	1	0

• B,C

- if BC=00 then F=0
- if BC=01 then F=1
- if BC=10 then F=A
- if BC=11 then F=A'

BC	00	01	10	11
	I_0	I_1	I_2	I_3
A=0 A'	0		2	
A=1 A	4			7
	0	1	A	A'

$I_0=0, I_1=1, I_2=A, I_3=A'$

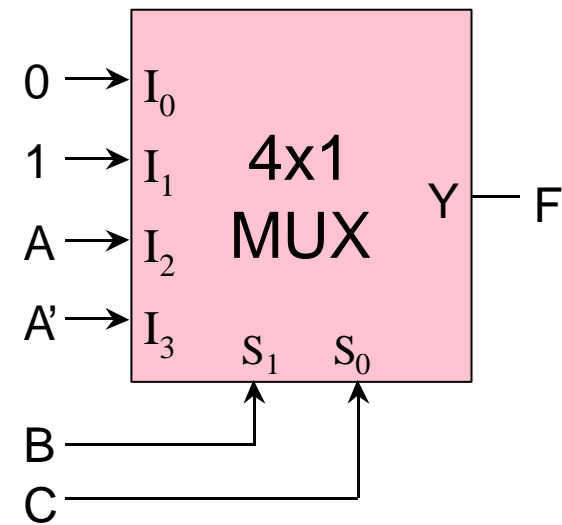

Multiplexer


Bool

() $F(A,B,C,D) = \Sigma(1,3,4,11,12,13,14,15)$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


A, B, C

	ABC	000	001	010	011	100	101	110	111
		I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇
D=0	D'	0	2	4	6	8	10	12	14
D=1	D	1	3	5	7	9	11	13	15
		D	D	D'	0	0	D	1	1

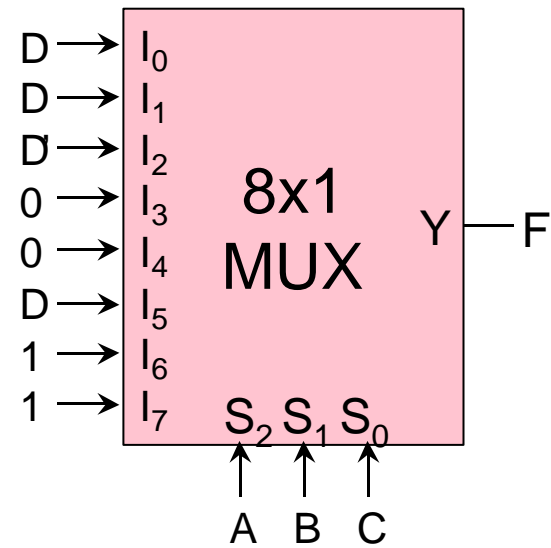


Demultiplexer(DMUX)

- 2^n
-

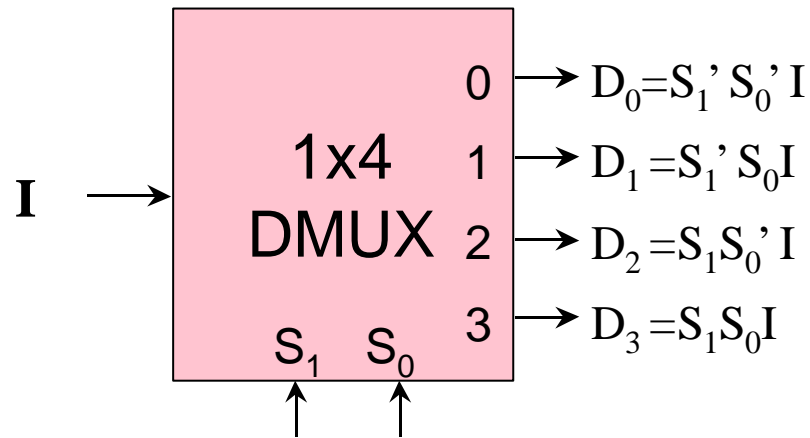


S_1	S_0	D_0	D_1	D_2	D_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

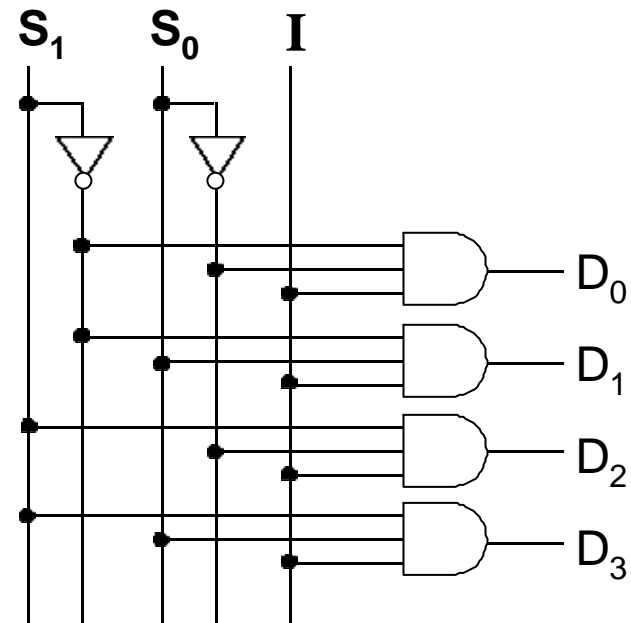

Demultiplexers as General-Purpose Logic

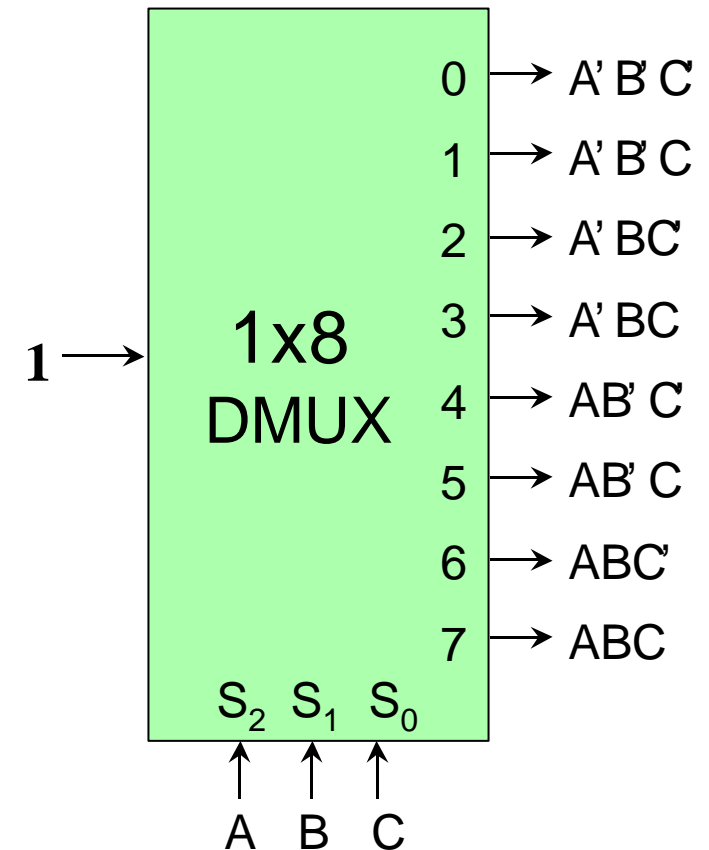- ❑ A 1×2^n DMUX can implement any function of n variables
 - ◆ Apply the variables as select inputs
 - ◆ Tie the enable input to a logic “1”
 - ◆ Sum the appropriate minterms
- ❑ DMUX decodes appropriate minterms from the control signals
- ❑ Decoder with enable is identical to DMUX




Demultiplexers as General-Purpose Logic

□ Examples

$$F1 = A'BC'D + A'B'CD + ABCD$$

$$F2 = ABC'D + ABC$$

$$F3 = A' + B' + C' + D'$$

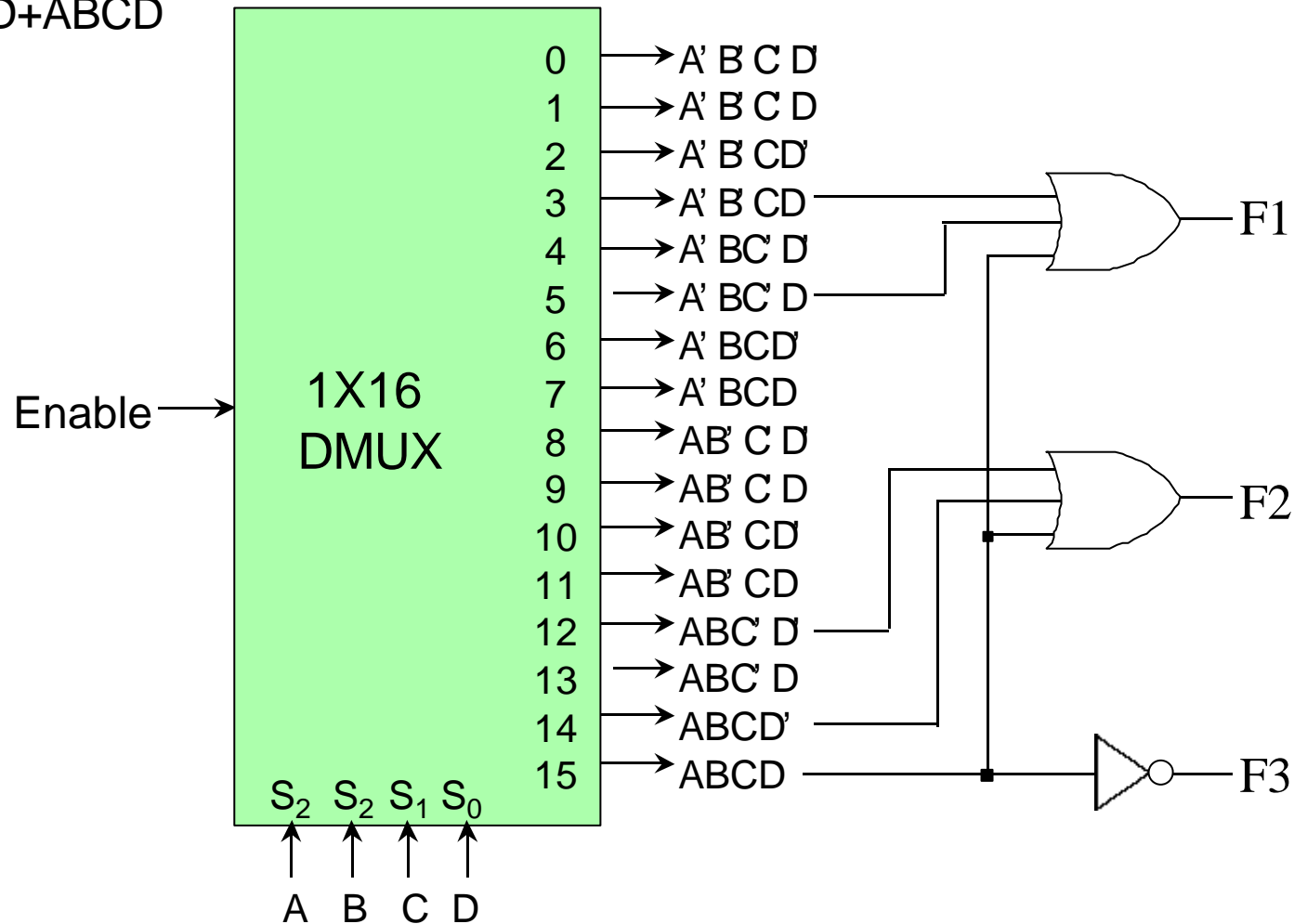

Cascading DMUX

□ 5x32 DMUX

◆ one 2x4 DMUX

◆ four 3x8 DMUX

